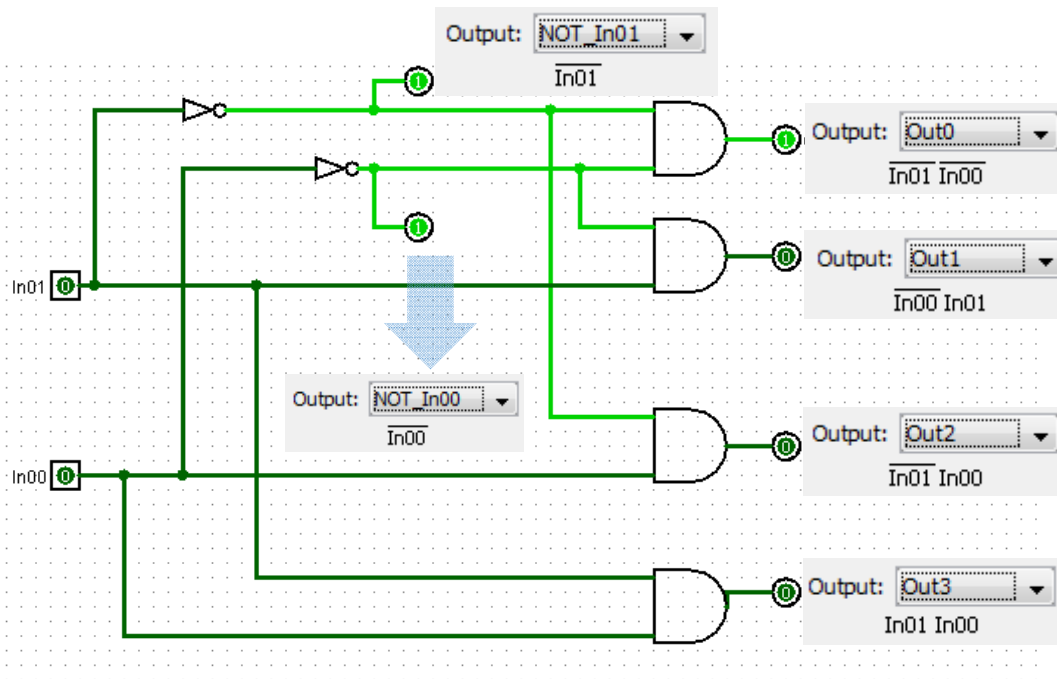


3. Combinational Circuits II

Aims

- to show how logic gates can be combined to produce useful circuits such as **decoders** and **adders**
- to show how individual combinational circuits can be combined to produce a simple **ALU**¹
- to introduce a simple **memory storage** device called a **register**

3.1 Decoders




- A **decoder** is a combinational circuit that converts binary information from n inputs to a maximum of 2^n unique outputs
- A decoder takes an n -bit number as input and uses it to select (set to 1) exactly **one** of the 2^n outputs

In00	In01	NOT_In00	NOT_In01	Out0	Out1	Out2	Out3
0	0	1	1	1	0	0	0
0	1	1	0	0	1	0	0
1	0	0	1	0	0	1	0
1	1	0	0	0	0	0	1

 3.1.1


Line Decoders

- For **each possible input combination** there are **seven** outputs that are equal to **0** and only one that is equal to **1**.
- The output equal to **1** represents the equivalent of the binary number that is applied to the inputs.



A	B	C	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

A	B	C	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

 


Application:
device selector





MOTOROLA SN54/74LS138

1-OF-8 DECODER/ DEMULTIPLEXER


LOGIC DIAGRAM

 


LOGIC SYMBOL

  

J SUFFIX
CERAMIC
CASE 620-09

 

N SUFFIX
PLASTIC
CASE 648-08

 


D SUFFIX
SOIC
CASE 751B-03

ORDERING INFORMATION

SN54LSXXXJ Ceramic
SN74LSXXXN Plastic
SN74LSXXXD SOIC

INPUTS						OUTPUTS							
E ₁	E ₂	E ₃	A ₀	A ₁	A ₂	O ₀	O ₁	O ₂	O ₃	O ₄	O ₅	O ₆	O ₇
H	X	X	X	X	X	H	H	H	H	H	H	H	H
X	H	X	X	X	X	H	H	H	H	H	H	H	H
X	X	L	X	X	X	H	H	H	H	H	H	H	H
L	L	H	L	L	L	H	H	H	H	H	H	H	H
L	L	H	L	L	L	H	L	H	H	H	H	H	H
L	L	H	L	L	L	H	H	L	H	H	H	H	H
L	L	H	L	L	L	H	H	H	L	H	H	H	H
L	L	H	L	L	L	H	H	H	H	L	H	H	H
L	L	H	L	L	L	H	H	H	H	H	L	H	H
L	L	H	L	L	L	H	H	H	H	H	H	L	H
L	L	H	L	L	L	H	H	H	H	H	H	H	L

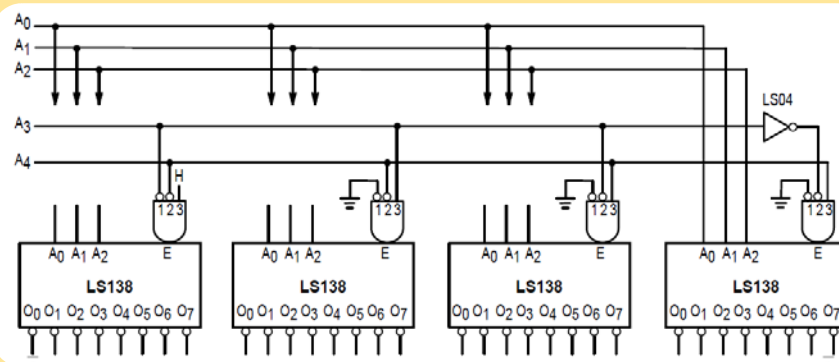
H = HIGH Voltage Level
L = LOW Voltage Level
X = Don't Care



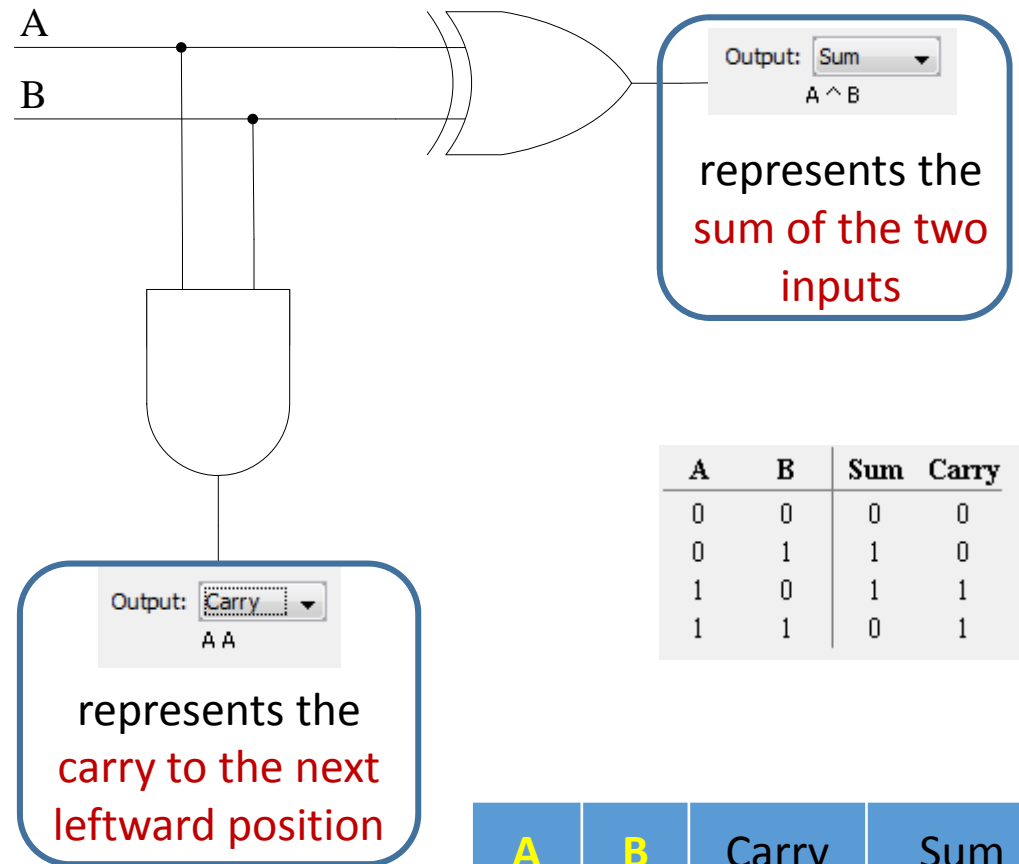3.2.1

Half Adder

- A **half adder** is an arithmetic circuit that performs the **addition of two bits**
- The circuit has **two inputs (A, B)** and **two outputs (Sum, Carry)**
- Two outputs are necessary**
because the
sum of two binary digits ranges from **0** to **2**
and
the binary equivalent of 2 requires **two** digits



The simple addition performed by a **half adder** can consist of **four** possible operations :

0+0	=	0
0+1	=	1
1+0	=	1
1+1	=	10


A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

3.2.2

Full Adder


- A full adder is a circuit that performs the **addition of three bits**
- The name of the circuit stems from the fact that **two half adders are joined together** to create a **full adder**
- The circuit has **three inputs** (A, B, Carry in) and **two outputs** (Sum, Carry out)

A	B	CarryIn	CarryOut	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


Two **outputs** are necessary because the **sum of three binary digits ranges from 0 to 3** and the binary equivalent of 2 or 3 requires **two digits**

A	B	Carry in	Carry out	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

 - To build an adder for **two 8-bit numbers** the full adder is replicated **eight times**



- The **carry out** of one full adder is used as the **carry in** into its left neighbour
 - The carry into the rightmost bit is set to 0.

This type of adder is called a


ripple carry adder

because the addition cannot complete until the carry has rippled all the way across the adders


SN7480 . . . J OR N PACKAGE

description

These single-bit, high-speed, binary full adders with gated complementary inputs, complementary sum (Σ and $\bar{\Sigma}$) outputs and inverted carry output are designed for medium-and high-speed, multiple-bit, parallel-add/serial-carry application. These circuits (see schematic) utilize diode-transistor logic (DTL) for the gated inputs, and high-speed, high-fan-out transistor-transistor logic (TTL) for the sum and carry outputs and are entirely compatible with the TTL logic families. The implementation of a single-inversion, high-speed, Darlington-connected serial-carry circuit minimizes the necessity for extensive "look-ahead" and carry-cascading circuits.

 

(DUAL-IN-LINE) [FLAT PACKAGE]

 

FUNCTION TABLE
(See Notes 1, 2, and 3)


INPUTS			OUTPUTS		
C_n	B	A	\bar{C}_{n+1}	$\bar{\Sigma}$	Σ
L	L	L	H	H	L
L	L	H	H	L	H
L	H	L	H	L	H
L	H	H	L	H	L
H	L	L	H	L	H
H	L	H	L	H	L
H	H	L	L	H	L
H	H	H	L	L	H

H = high level, L = low level

NOTES: 1. $A = \bar{A}_C + \bar{A}^* + A1 \cdot A2$, $B = \bar{B}_C + \bar{B}^* + B1 \cdot B2$.


2. When A* is used as an input, A1 or A2 must be low. When B* is used as an input, B1 or B2 must be low.

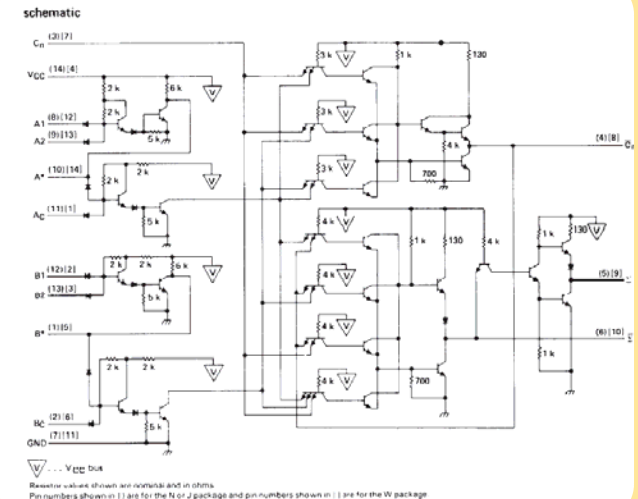3. When A1 and A2 or B1 and B2 are used as inputs, A* or B*, respectively, must be open or used to perform dot-AND logic.




74 83A Full Adder

LOGIC DIAGRAM

 

LOGIC SYMBOL

 

FUNCTIONAL TRUTH TABLE

C (n-1)	A _n	B _n	Σ _n	C _n
L	L	L	L	L
L	L	H	H	L
L	H	L	H	L
L	H	H	L	H
H	L	L	H	L
H	L	H	L	H
H	H	L	L	H
H	H	H	H	H

C₁ — C₃ are generated internally
C₀ — is an external input
C₄ — is an output generated internally

FUNCTIONAL DESCRIPTION

The LS83A adds two 4-bit binary words (A plus B) plus the incoming carry. The binary sum appears on the sum outputs (Σ₁–Σ₄) and outgoing carry (C₄) outputs.

$$C_0 + (A_1+B_1)+2(A_2+B_2)+4(A_3+B_3)+8(A_4+B_4) = \Sigma_1+2\Sigma_2+4\Sigma_3+8\Sigma_4+16C_4$$

Where: (+) = plus

Due to the symmetry of the binary add function the LS83A can be used with either all inputs and outputs active HIGH (positive logic) or with all inputs and outputs active LOW (negative logic). Note that with active HIGH Inputs, Carry Input can not be left open, but must be held LOW when no carry in is intended.

Example


	C ₀	A ₁	A ₂	A ₃	A ₄	B ₁	B ₂	B ₃	B ₄	Σ ₁	Σ ₂	Σ ₃	Σ ₄	C ₄	
Logic Levels	L	L	H	L	H	H	L	L	H	H	H	L	L	H	
Active HIGH	0	0	1	0	1	1	0	0	1	1	1	0	0	1	(10+9 = 19)
Active LOW	1	1	0	1	0	0	1	1	0	0	0	1	1	0	(carry+5+6 = 12)

4.1 ALU – Arithmetic Logic Unit


The heart of every computer is a processor,
Or **CPU** (Central Processing Unit)

CPU consists of an **ALU** and a **Control Unit**

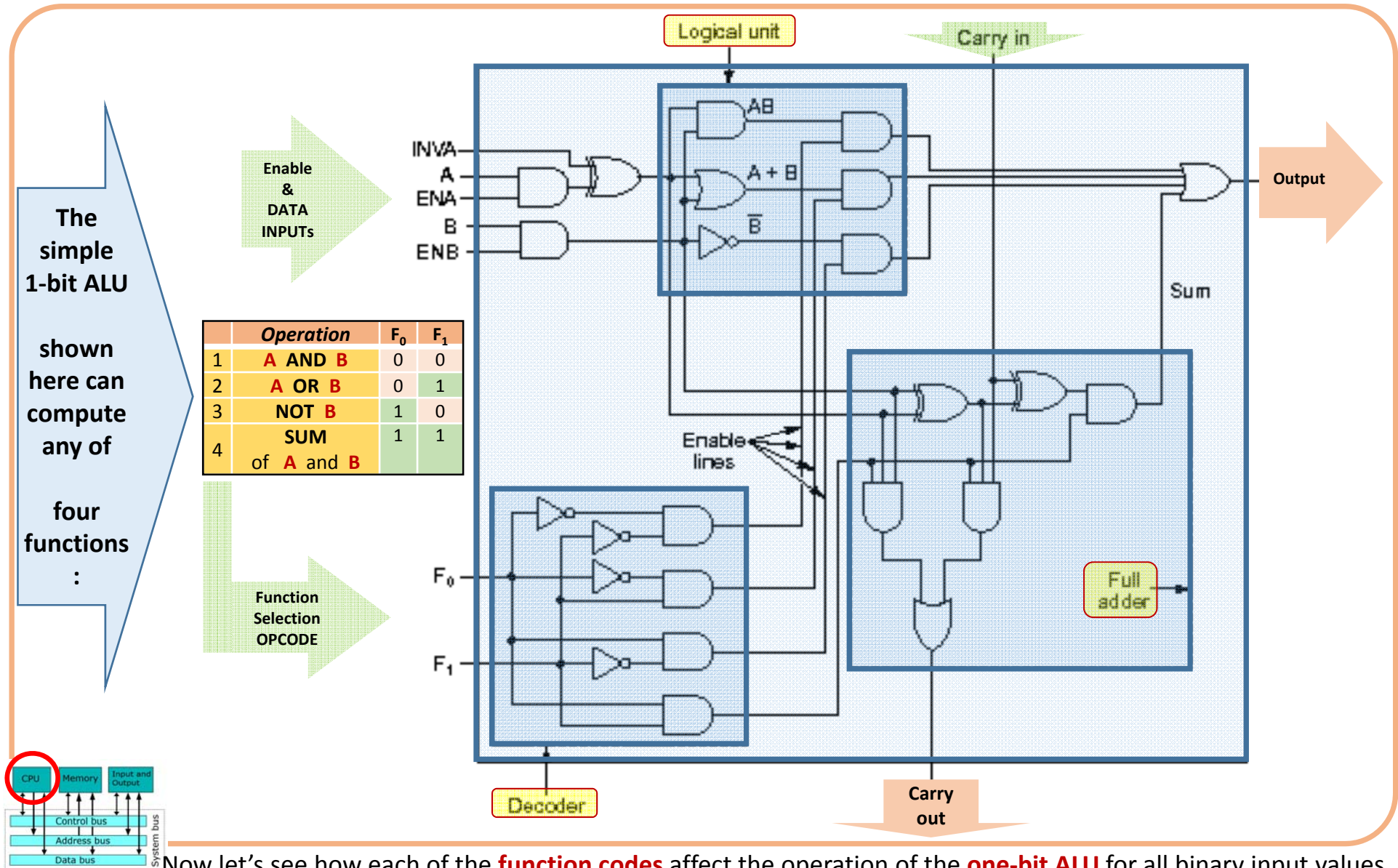
The **ALU** is a circuit, used in the **CPU** for performing **Arithmetic and (Boolean) Logical operations**



1 bit ALU		INPUTS				OUTPUTS		
A	B	F ₁	F ₀	ENA	ENB	INVA	CARRY IN	CARRY OUTPUT OUTPUT
0	0	0	0	1	1	0	0	0

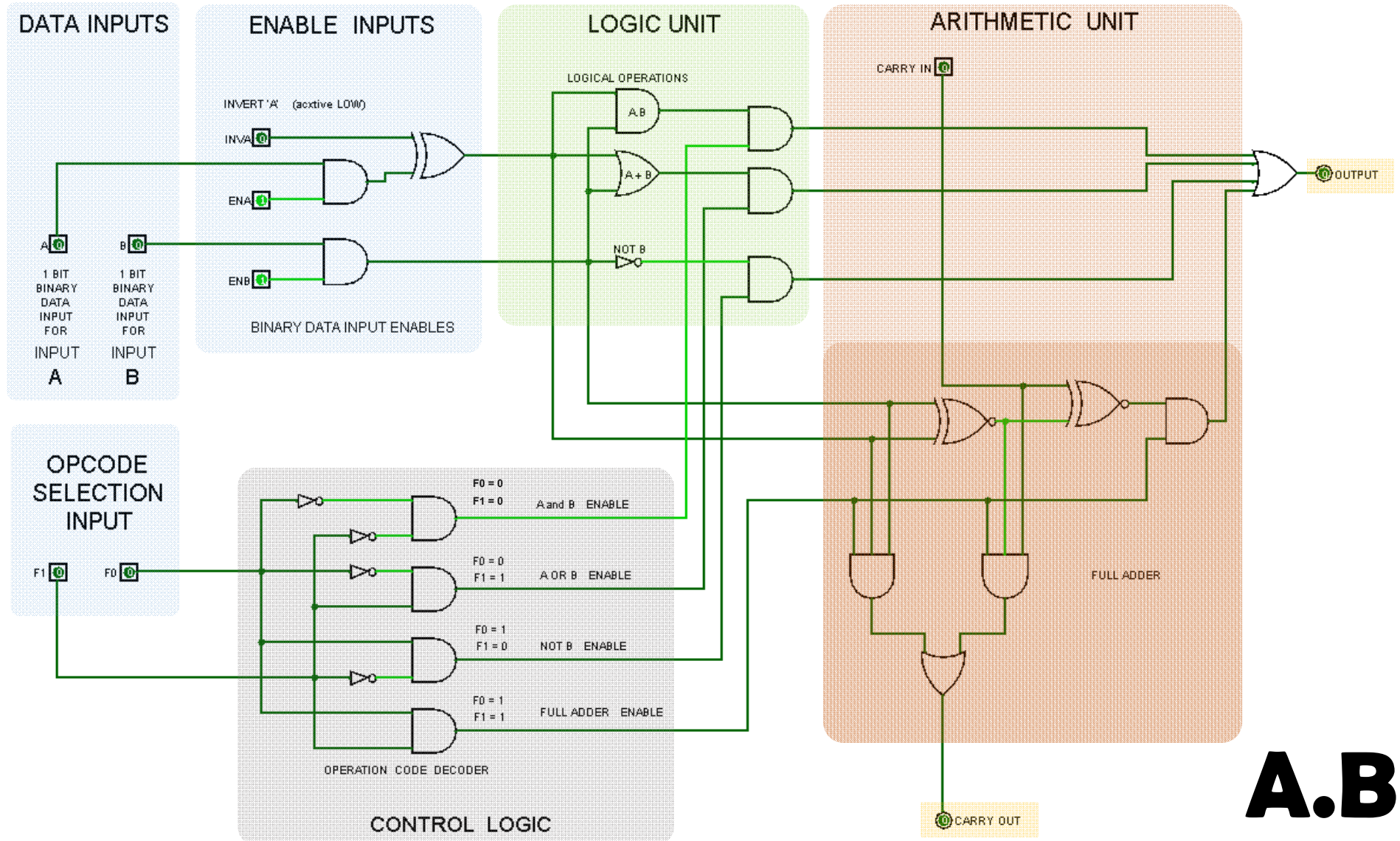


1 bit ALU		INPUTS				OUTPUTS		
A	B	F ₁	F ₀	ENA	ENB	INVA	CARRY IN	CARRY OUTPUT OUTPUT
0	1	0	0	1	1	0	0	0 0

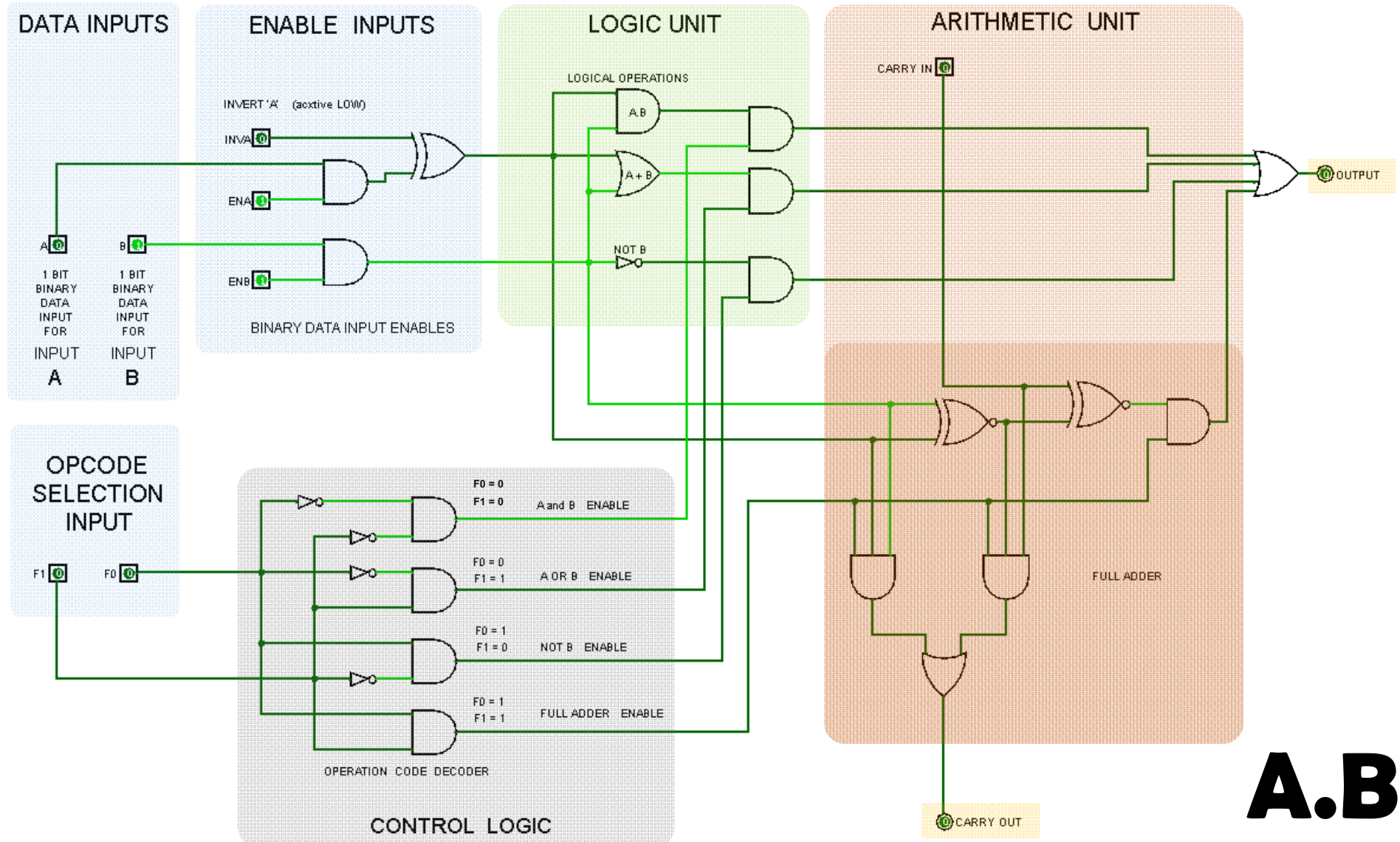


A.B

1 bit ALU		INPUTS				OUTPUTS		
A	B	F ₁	F ₀	ENA	ENB	INVA	CARRY IN	CARRY OUTPUT OUTPUT
1	0	0	0	1	1	0	0	0

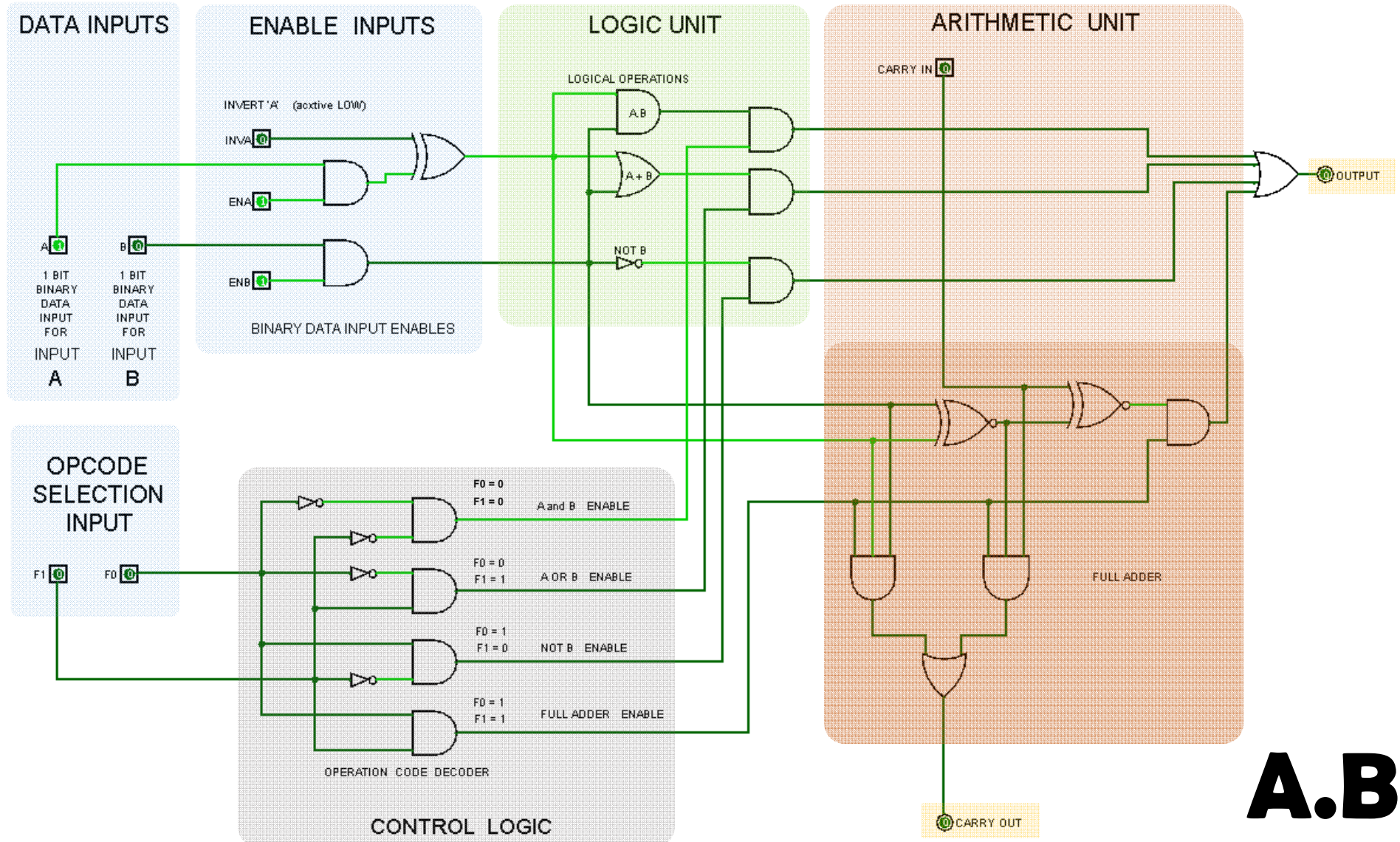


A.B

1 bit ALU		INPUTS				OUTPUTS		
A	B	F ₁	F ₀	ENA	ENB	INVA	CARRY IN	CARRY OUTPUT OUTPUT
1	1	0	0	1	1	0	0	0 1

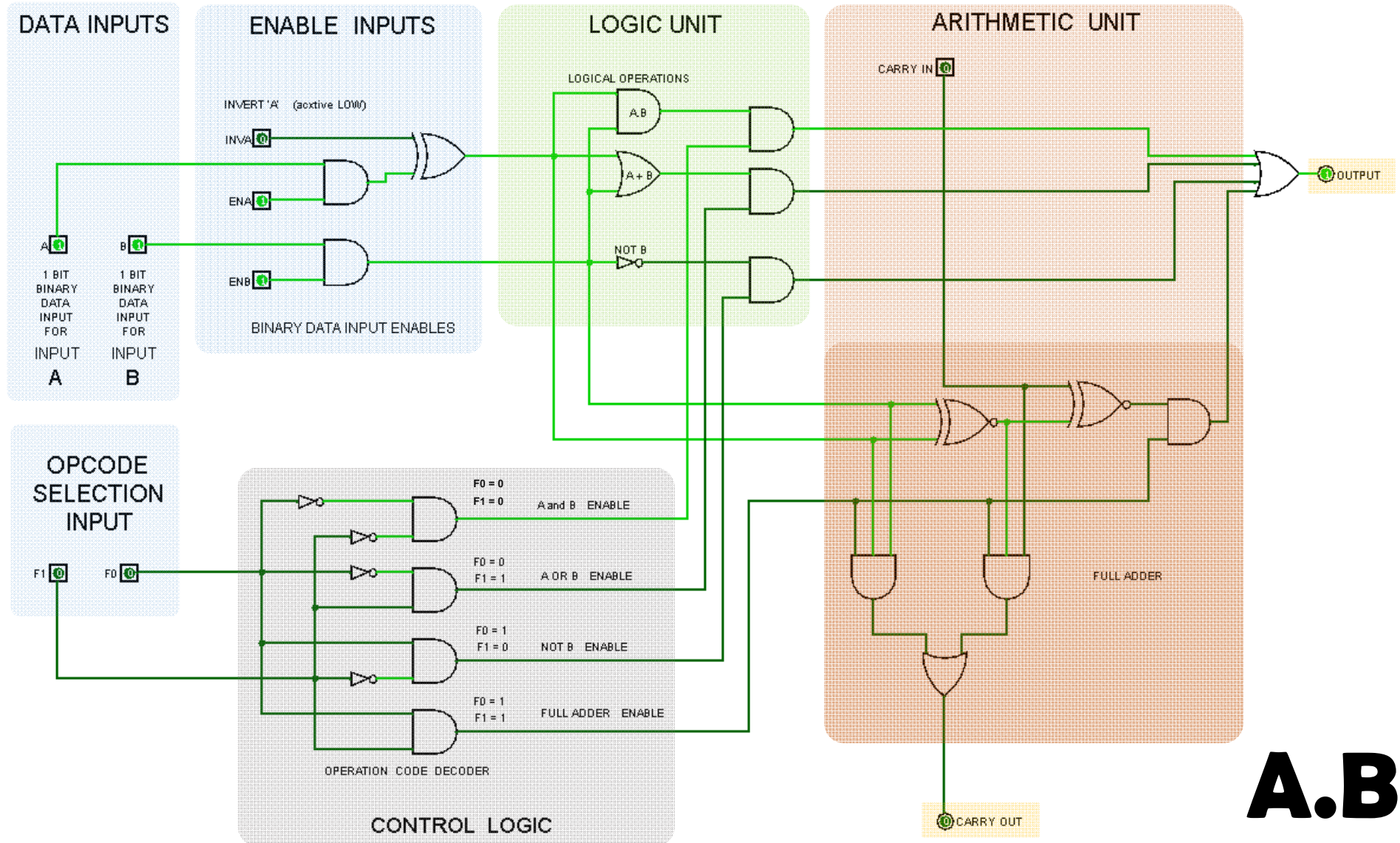


1 bit ALU		INPUTS				OUTPUTS		
A	B	F ₁	F ₀	ENA	ENB	INVA	CARRY IN	CARRY OUTPUT OUTPUT
0	0	0	1	1	1	0	0	0 1

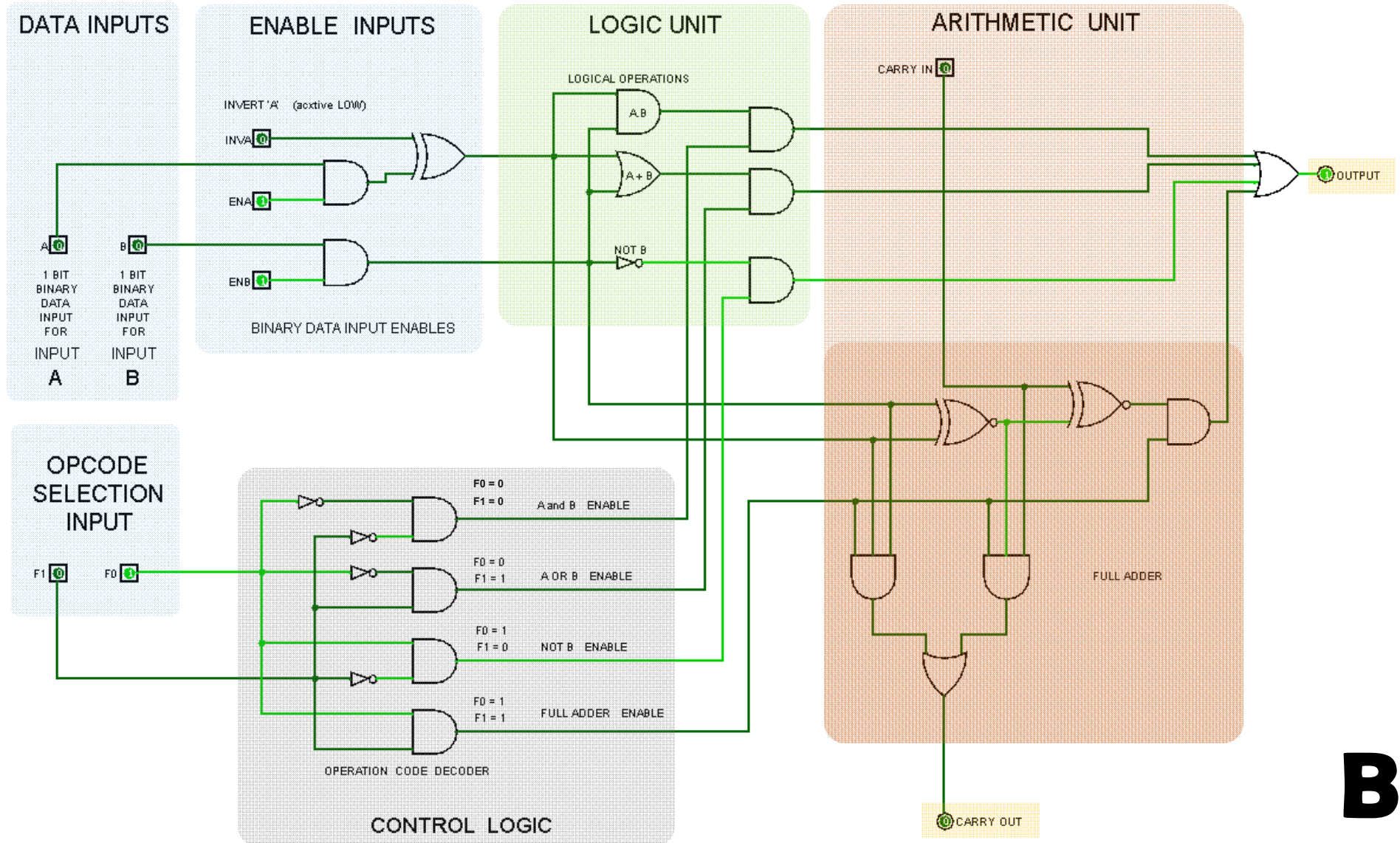


B

1 bit ALU		INPUTS				OUTPUTS		
A	B	F ₁	F ₀	ENA	ENB	INVA	CARRY IN	CARRY OUTPUT OUTPUT
0	1	0	1	1	1	0	0	0

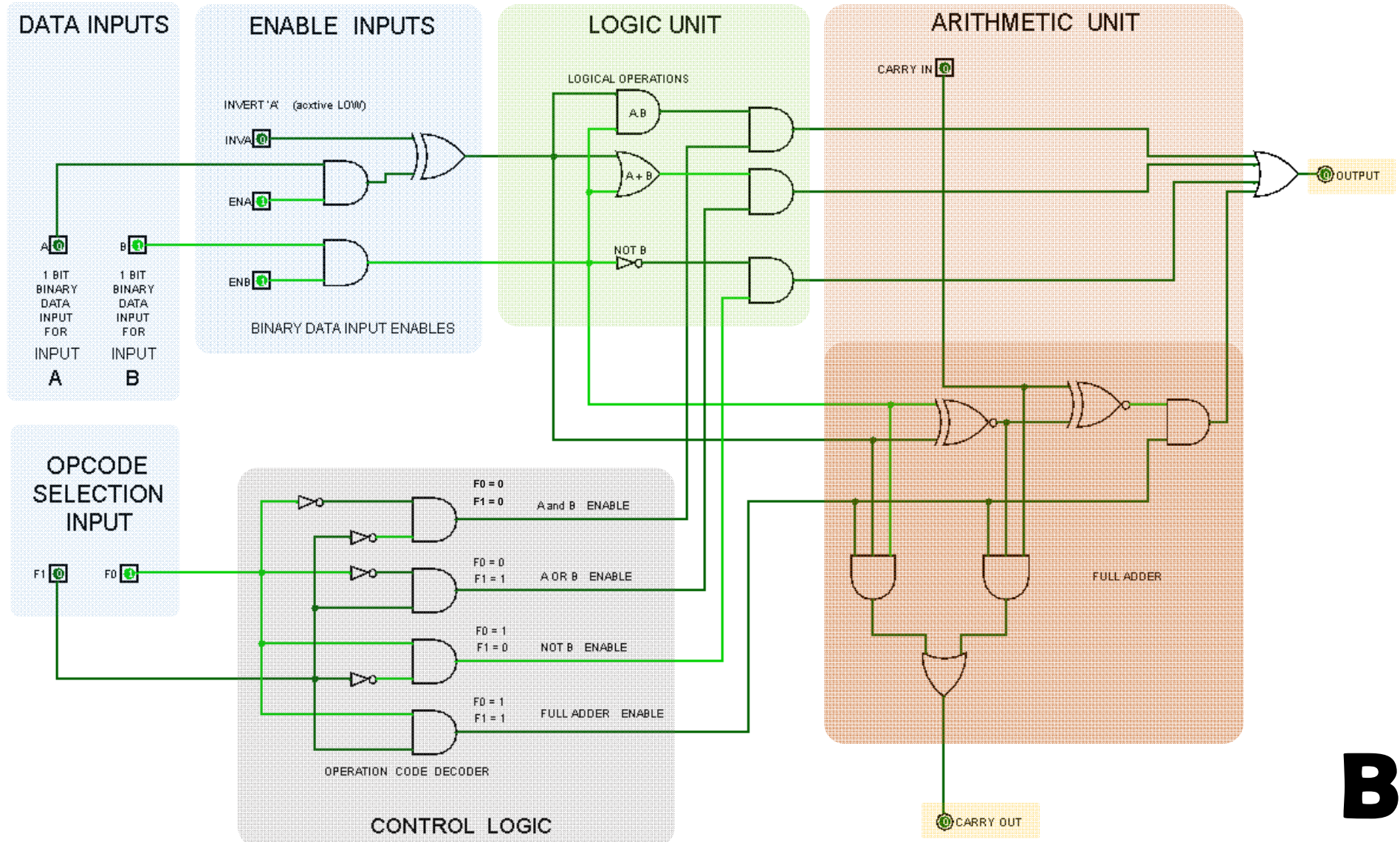


B

1 bit ALU		INPUTS				OUTPUTS		
A	B	F ₁	F ₀	ENA	ENB	INVA	CARRY IN	CARRY OUTPUT OUTPUT
1	0	0	1	1	1	0	0	0 1

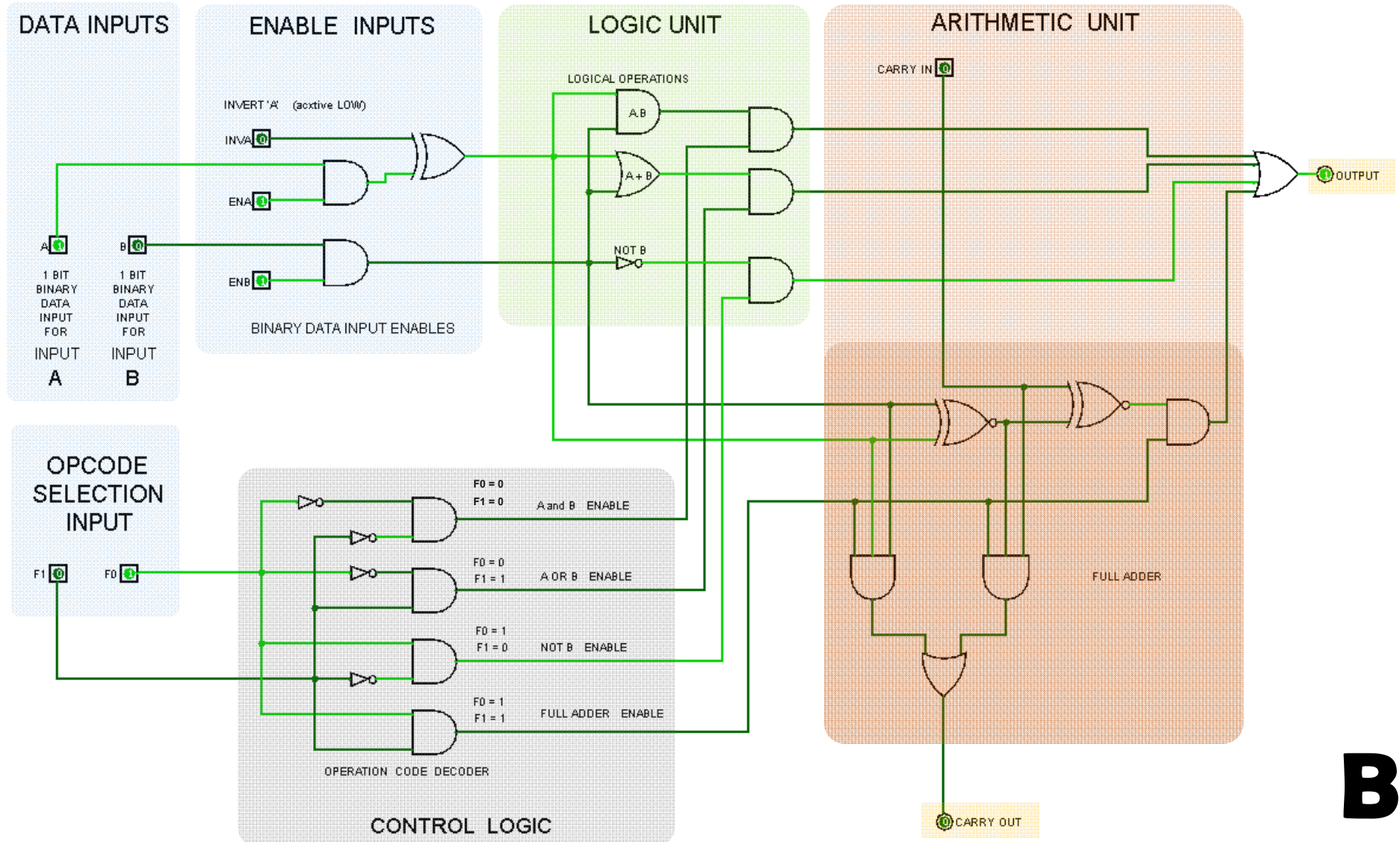


B

1 bit ALU		INPUTS				OUTPUTS		
A	B	F ₁	F ₀	ENA	ENB	INVA	CARRY IN	CARRY OUTPUT OUTPUT
1	1	0	1	1	1	0	0	0

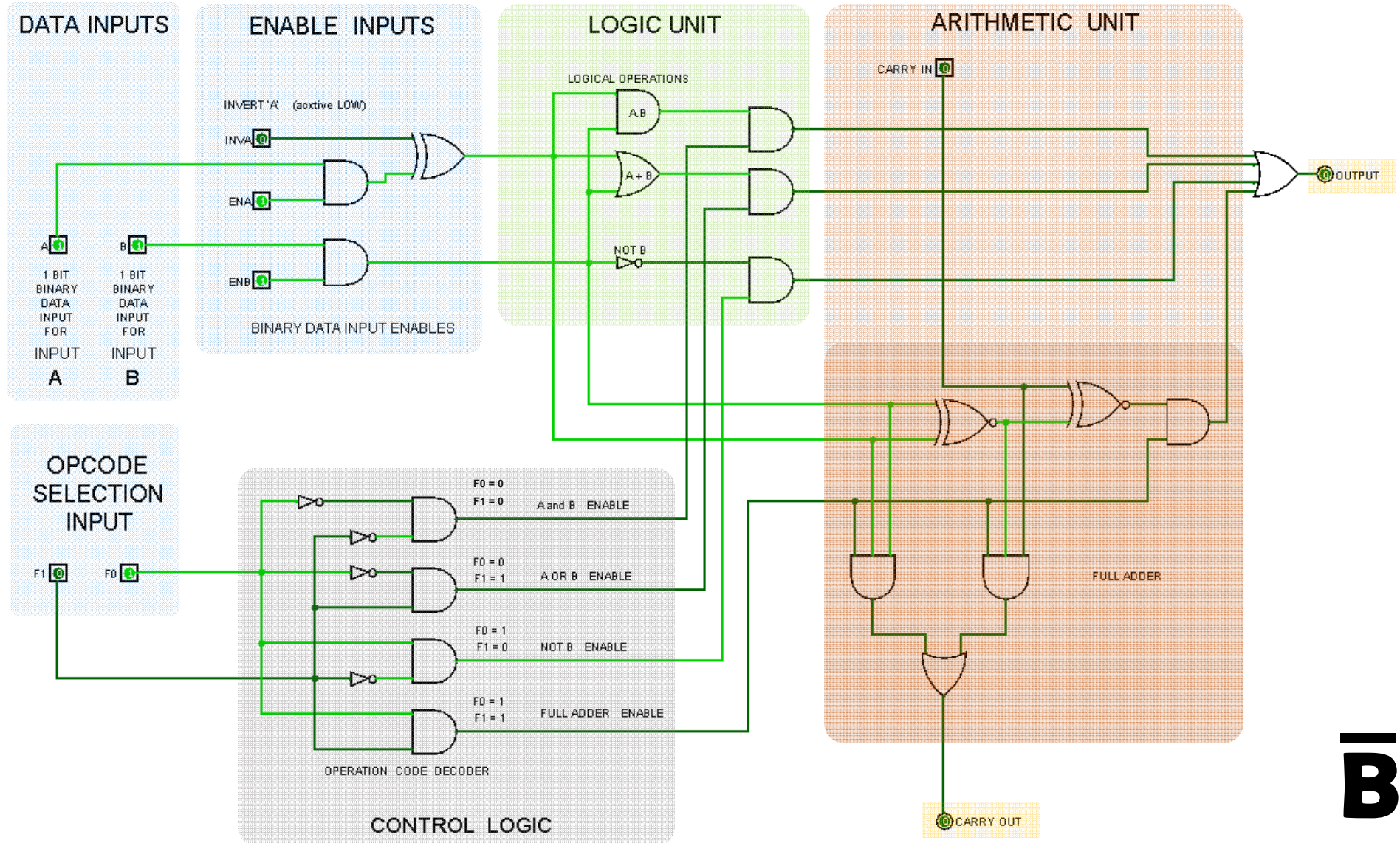


B

1 bit ALU		INPUTS				OUTPUTS		
A	B	F ₁	F ₀	ENA	ENB	INVA	CARRY IN	CARRY OUTPUT OUTPUT
0	0	1	0	1	1	0	0	0

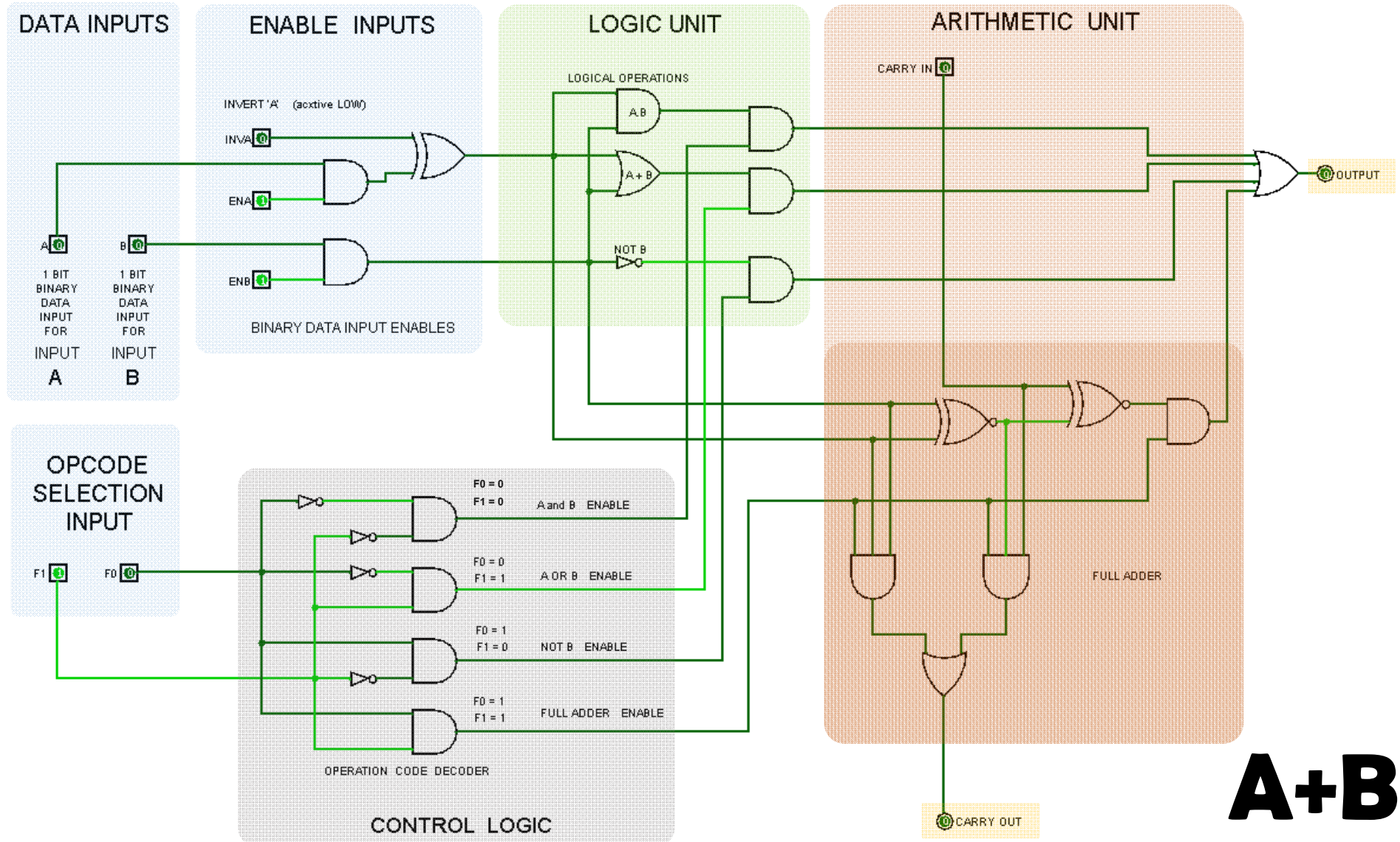


1 bit ALU		INPUTS				OUTPUTS		
A	B	F ₁	F ₀	ENA	ENB	INVA	CARRY IN	CARRY OUTPUT OUTPUT
0	1	1	0	1	1	0	0	1

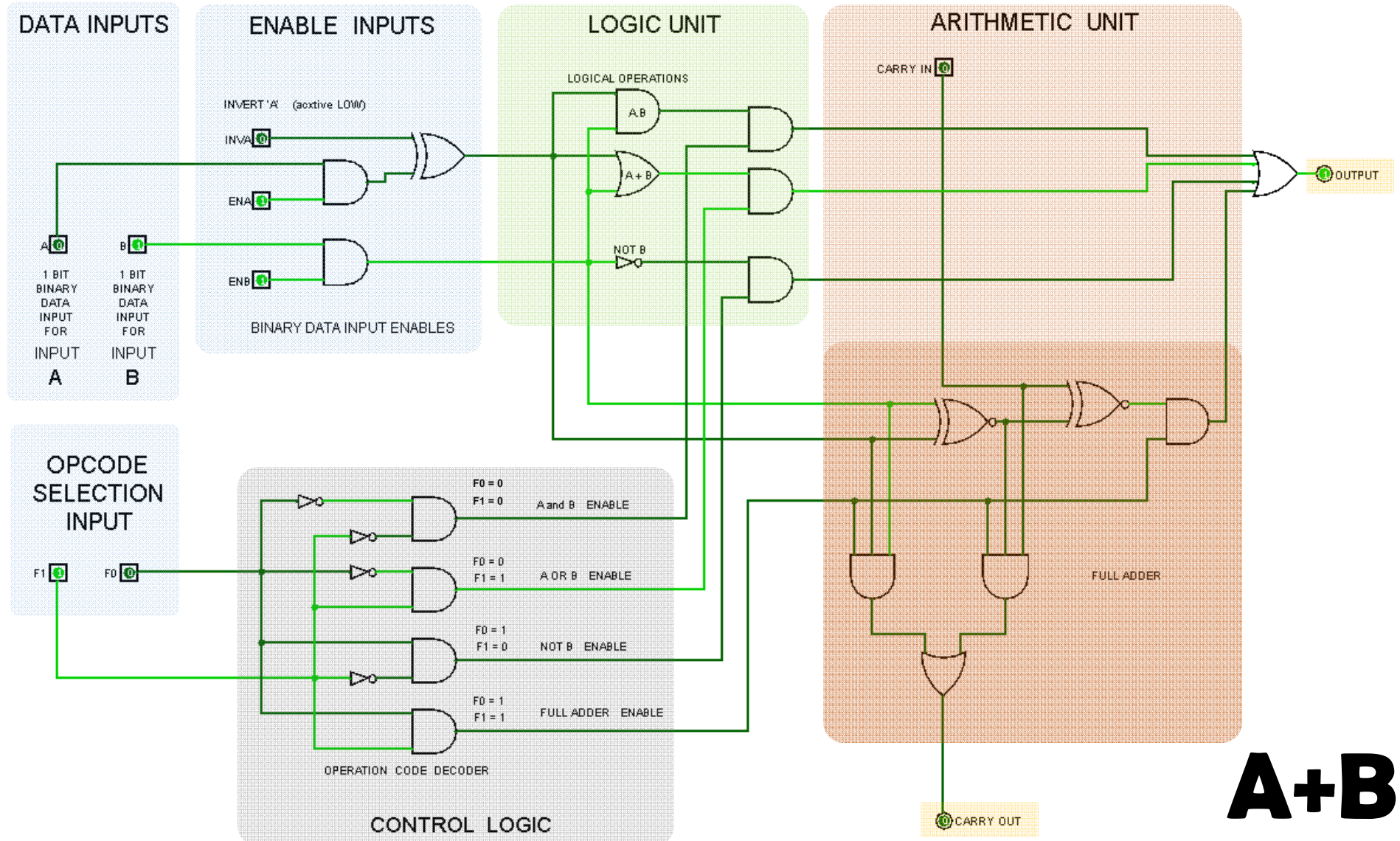


A+B

1 bit ALU		INPUTS				OUTPUTS		
A	B	F ₁	F ₀	ENA	ENB	INVA	CARRY IN	CARRY OUTPUT OUTPUT
1	0	1	0	1	1	0	0	1

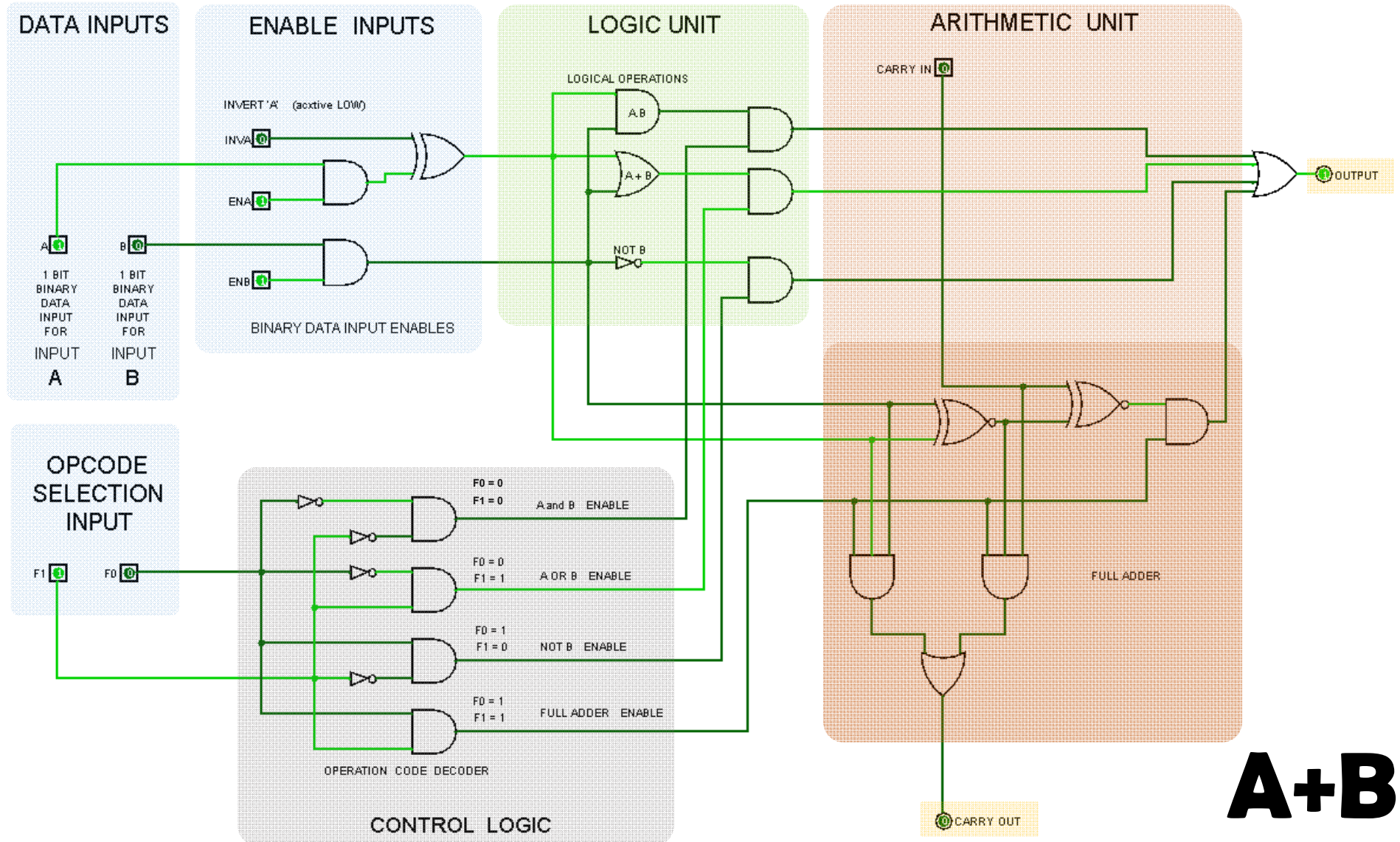


1 bit ALU		INPUTS				OUTPUTS		
A	B	F ₁	F ₀	ENA	ENB	INVA	CARRY IN	CARRY OUTPUT OUTPUT
1	1	1	0	1	1	0	0	0 1

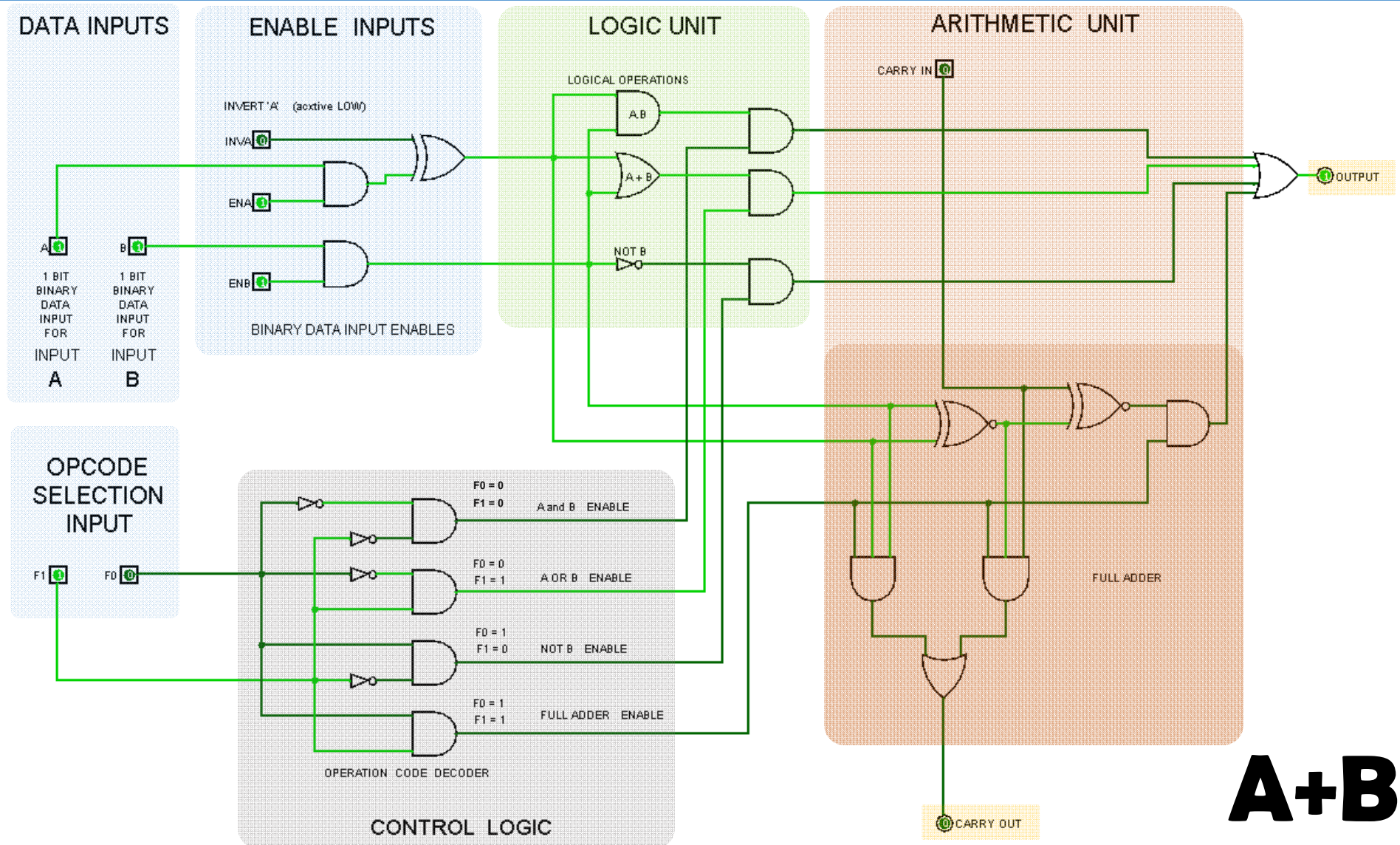


A+B


1 bit ALU		INPUTS				OUTPUTS		
A	B	F ₁	F ₀	ENA	ENB	INVA	CARRY IN	CARRY OUTPUT OUTPUT
0	0	1	1	1	1	0	0	0

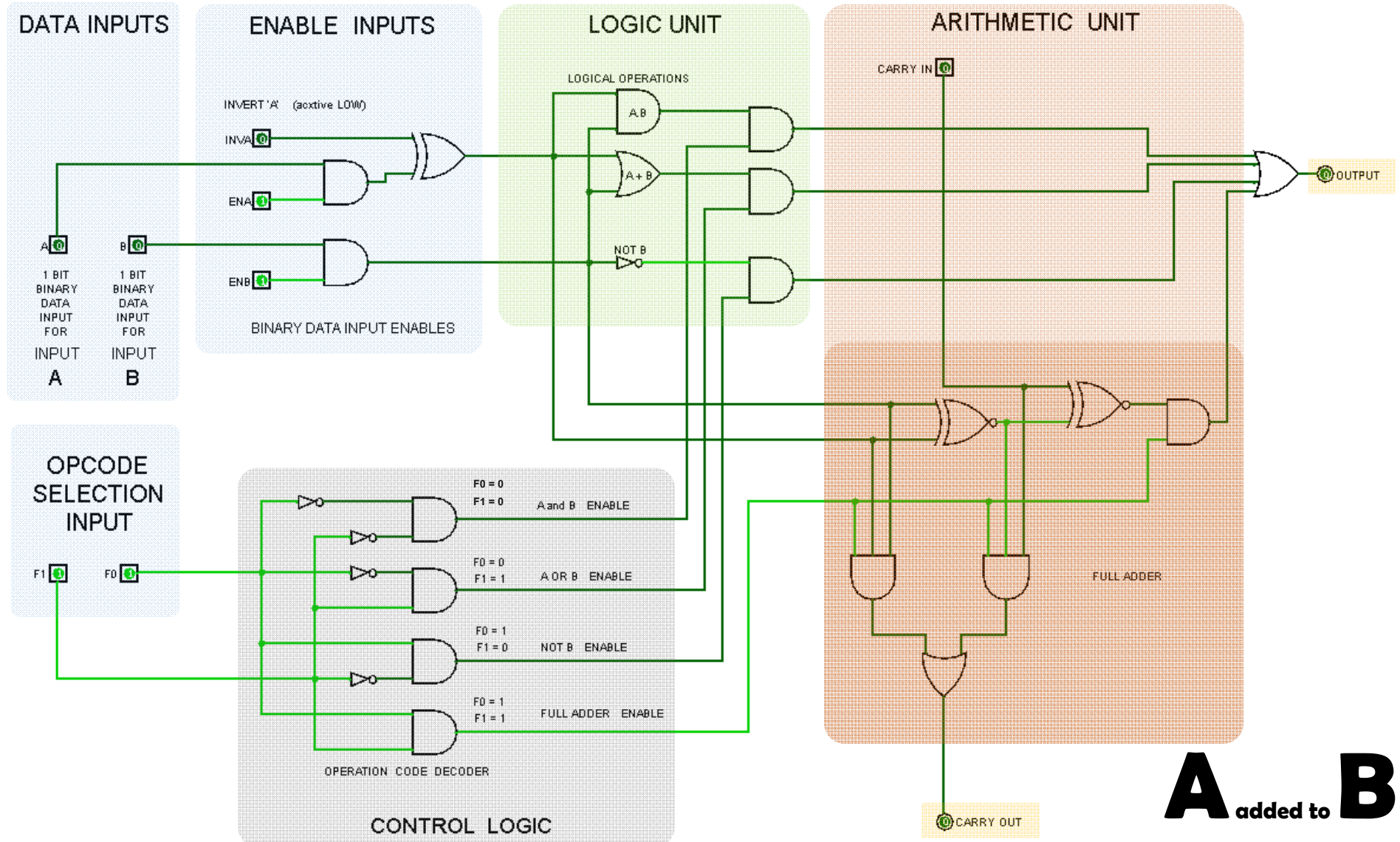


1 bit ALU		INPUTS				OUTPUTS		
A	B	F ₁	F ₀	ENA	ENB	INVA	CARRY IN	CARRY OUTPUT OUTPUT
0	1	1	1	1	1	0	0	0 1

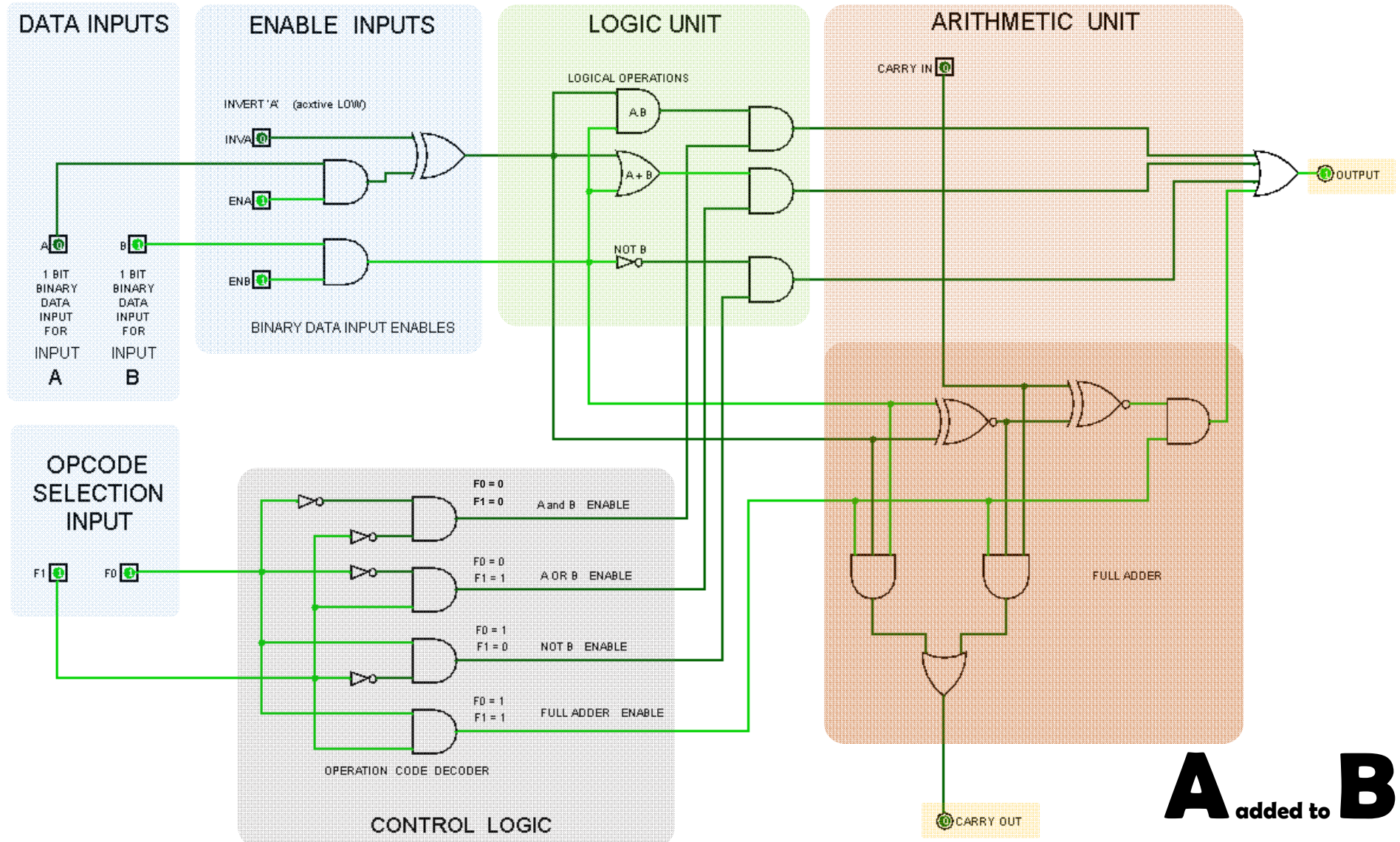

1 bit ALU		INPUTS				OUTPUTS		
A	B	F ₁	F ₀	ENA	ENB	INVA	CARRY IN	CARRY OUTPUT OUTPUT
1	0	1	1	1	1	0	0	0 1

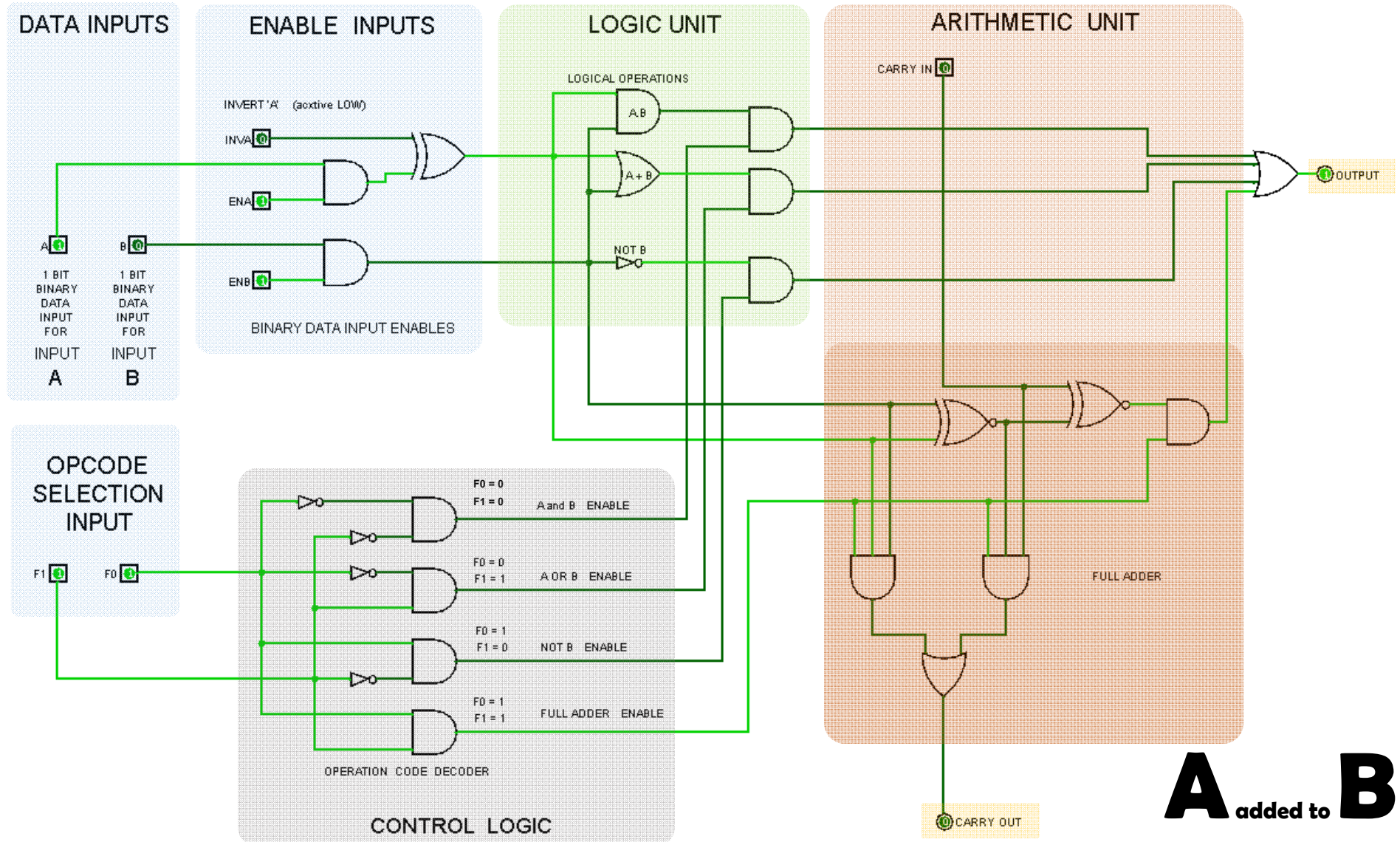


1 bit ALU		INPUTS				OUTPUTS		
A	B	F ₁	F ₀	ENA	ENB	INVA	CARRY IN	CARRY OUTPUT OUTPUT
1	1	1	1	1	1	0	0	1 0

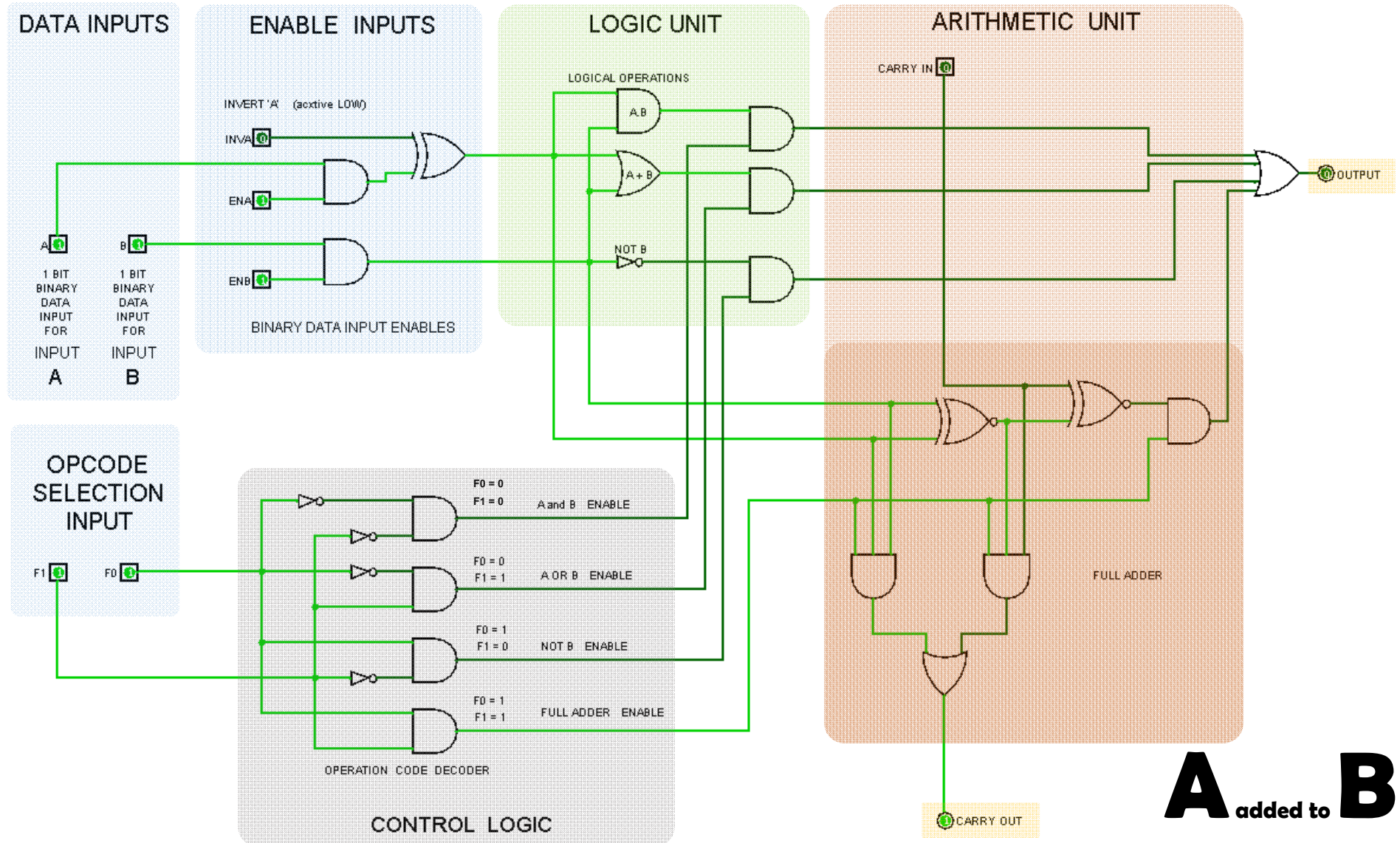



A added to B

 1-bit ALUs allow computer designers to build an ALU of any desired size





When present it increments (adds 1) to the result,
allowing the computation of sums such as **$A+1$**

Common symbol used for an ALU

  

74181

bit slice Arithmetic & Logic Unit

 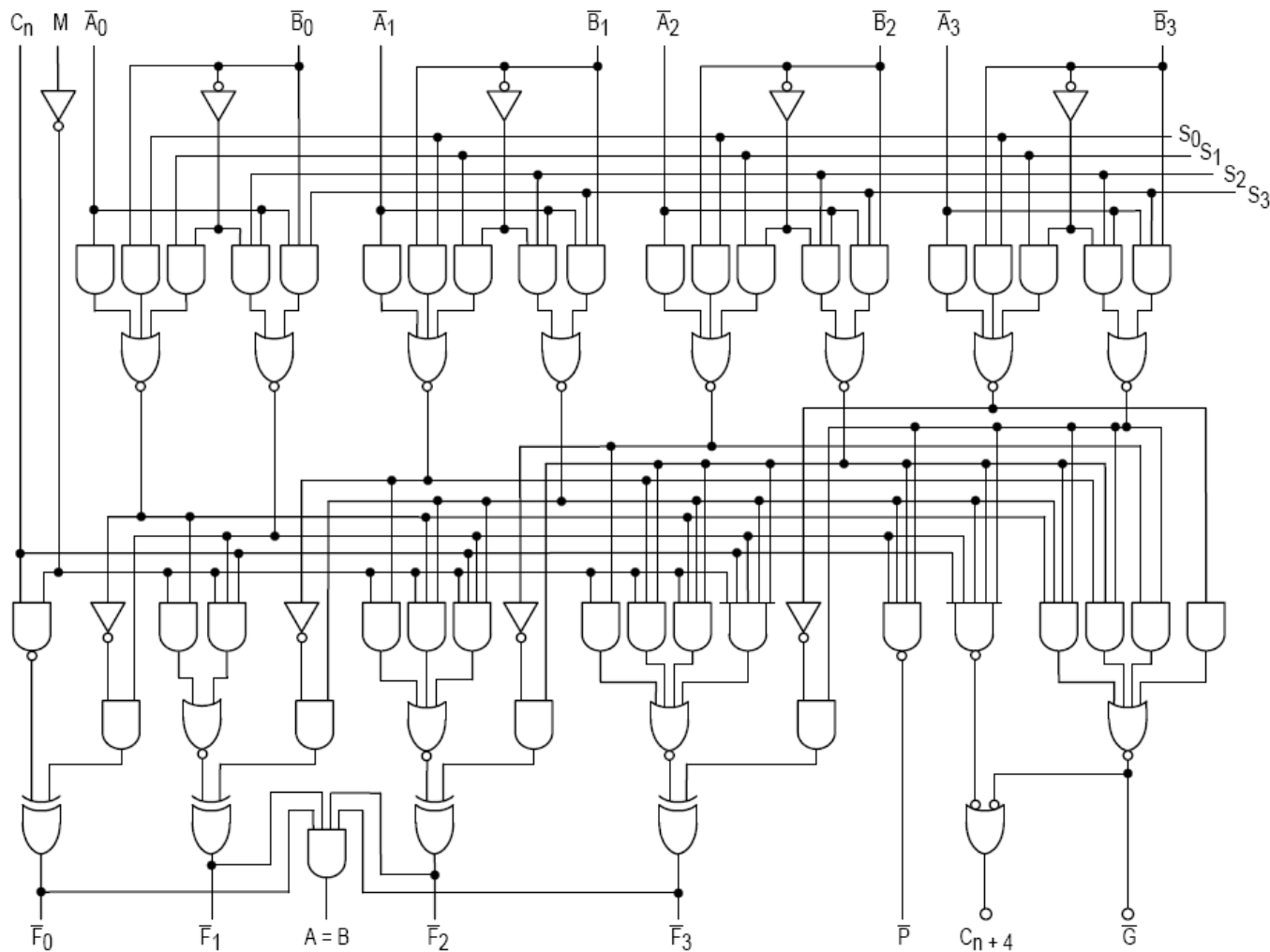

4.2 Memory

Combinational circuits

- *outputs dependent on* ***present input values***

Sequential circuits

- *outputs depend on* ***present input values,*** and on ***past input values***

4.2.1 Flip-Flops

- Sequential circuit that forms the basic building block of memory
 - **stores a single bit**

Flip

:

output changes from

Flop

:


output changes from

D-type Flip-Flops


Two inputs:

- D** is the **data** input value (the data bit that the flip-flop is to store)
- EN** is the **enable** control input.

Standard symbol
74 79

 

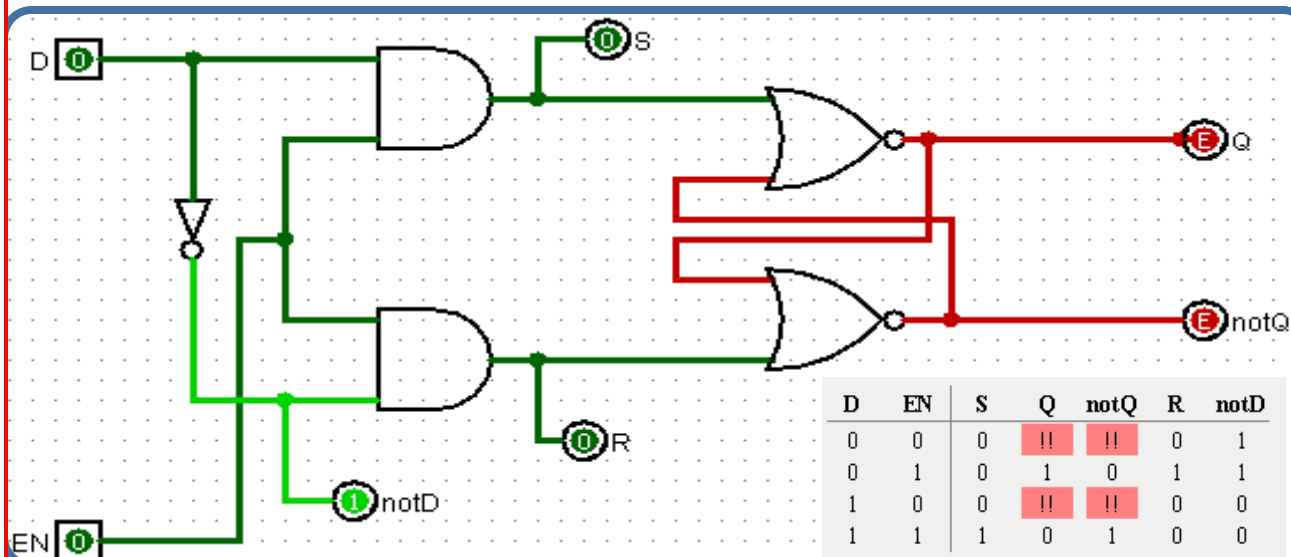- Output **Q** only changes on the transition of **EN** signal from one specified logic level to the other logic level.
 - without a transition the output will not change even if the input **D** does.
 - This is known as “**edge triggering**”
 - **positive** (0 to 1) vs **negative** (1 to 0) edge triggering.
- Operation of the flip-flop can be clarified by a



EN	D	Q
0	0	Q
0	1	Q
1	0	0
1	1	1

Operation of the flip-flop can be clarified by a simplified truth table.


Q output becomes the value of **D** after the activating transition of the **EN** signal.

4.2.3

Registers

CPU also contains *registers*

 - small, high-speed memory used to store temporary results and control information
- each register holds one value
- To store **eight bits**, **eight flip-flops** must be combined



$EN = 0$

- flip-flops do not record the data being input to them, **Q** outputs remain unchanged

$EN = 1$

- flip-flops record the data on their **D** inputs and output it to their **Q** outputs

EN returns to 0

- **Q** outputs do not change and the data remains frozen in the flip-flops

References

- <http://ece-research.unm.edu/pollard/classes/338/lademo/LookAheadDemo.htm>