

5. Karnaugh Maps

5.1 A Three-Input Truth Table

Here is a truth table:

A	B	C	W	X	Y	Z
0	0	0	1	0	1	1
0	0	1	1	1	1	0
0	1	0	0	1	1	1
0	1	1	1	0	0	0
1	0	0	1	1	1	0
1	0	1	0	0	0	1
1	1	0	1	0	0	0
1	1	1	1	1	0	1

5.2 Exercises

1. Draw and group the Karnaugh Map for **W**.
Derive the expression for **W**.
2. Draw and group the Karnaugh Map for **X**.
Derive the expression for **X**.
3. Draw and group the Karnaugh Map for **Y**.
Derive the expression for **Y**.
4. Draw and group the Karnaugh Map for **Z**.
Derive the expression for **Z**.

5.3 A Four-Input Truth Table

Here is a truth table:

A	B	C	D	P	Q	R	S
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	0	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	1
1	1	1	0	0	1	1	0
1	1	1	1	1	0	0	1

5.4 Exercises

5. Draw and group the Karnaugh Map for **P**.
Derive the expression for **P**.
6. Draw and group the Karnaugh Map for **Q**.
Derive the expression for **Q**.
7. Draw and group the Karnaugh Map for **R**.
Derive the expression for **R**.
8. Draw and group the Karnaugh Map for **S**.
Derive the expression for **S**.

