

## Combinational Circuits II

### Aims


- to show how logic gates can be combined to produce useful circuits such as decoders and adders
- to show how individual combinational circuits can be combined to produce a simple ALU
- to introduce a simple memory storage device called a register

### 3.1 Decoders

A **decoder** is a combinational circuit that converts binary information from  $n$  inputs to a maximum of  $2^n$  unique outputs.

- A decoder takes an  $n$ -bit number as input and uses it to select (set to 1) exactly one of the  $2^n$  outputs.

Below is a **2-to-4 decoder**

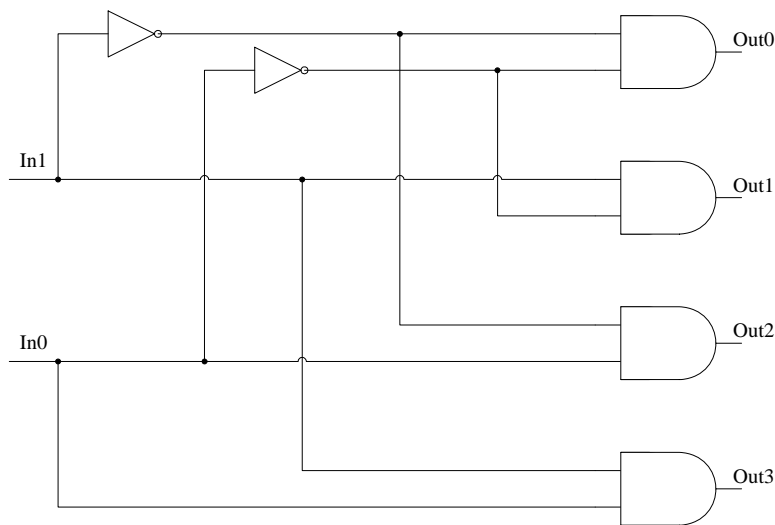

In0	In1	$\overline{\text{In0}}$	$\overline{\text{In1}}$	Out0	Out1	Out2	Out3
0	0						
0	1						
1	0						
1	1						

#### SAQ 3.1

1. How many outputs does a 2-input decoder have?
2. How many outputs does a 3-input decoder have?
3. How many outputs does a 4-input decoder have?
4. What is the purpose of a decoder?


answer

### 3.1.1 Line Decoder

The circuit below is a **3-to-8 decoder** and its operation is straightforward.

- Each **AND** gate has three inputs (the first is either **A** or  $\bar{A}$ , the second is either **B** or  $\bar{B}$ , and the third is either **C** or  $\bar{C}$ )
- Each gate is enabled by a different combination of inputs :

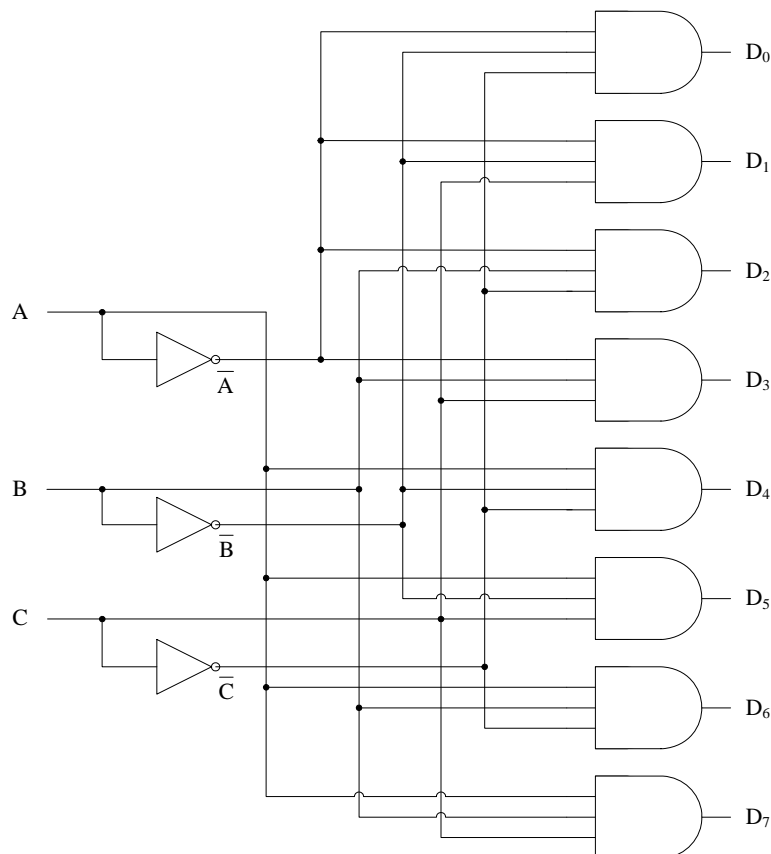$D_0$  by  $\bar{A} \bar{B} \bar{C}$ ,  $D_1$  by  $\bar{A} \bar{B} C$  etc.



The operation of the **3-to-8 (line) decoder** can be clarified from the truth table (right).



For each possible input combination there are seven outputs that are equal to **0** and only one that is equal to **1**.

The output equal to **1** represents the equivalent of the binary number that is applied to the inputs.

A	B	C	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

An application of a decoder is as a **device selector**.

- If, for example, a system has eight devices and only one can be in use at any instant, the inputs to the decoder can be used to select which device is used.

## 3.2 Adders

A computer that cannot **add integers** is unthinkable.

- Consequently, a circuit for performing addition is an essential part of every **CPU**.

### 3.2.1 Half Adder

A **half adder** is an arithmetic circuit that performs the **addition of two bits**.


The circuit has two inputs ( **A, B** ) and two outputs ( **Sum, Carry** ).

- Two outputs are necessary because the **sum** of two binary digits ranges from 0 to 2, and the binary equivalent of 2 requires two digits.

The **sum output** represents the **sum** of the two inputs while the **carry output** represents the **carry** to the next leftward position.

The simple addition performed by a **half adder** can consist of four possible operations:

0+0	=	0
0+1	=	1
1+0	=	1
1+1	=	10

 

A	B	Carry	Sum
0	0		
0	1		
1	0		
1	1		

- The carry output is **1** only when both inputs are **1**.
- The sum output is **1** only when either of the inputs are **1** (the sum output represents the least significant bit of the sum).

The boolean algebra representation of the two outputs is:

$$\begin{aligned} \text{Sum} &= A \oplus B \\ \text{Carry} &= A \cdot B \end{aligned}$$


### 3.2.2 Full Adder

A **full adder** is a circuit that performs the **addition of three bits**.

- The name of the circuit stems from the fact that two half adders are joined together to create a full adder.

The circuit has three inputs ( **A, B, Carry in** ) and two outputs ( **Sum, Carry out** ).

 - Two outputs are necessary because the sum of three binary digits ranges from 0 to 3, and the binary equivalent of 2 or 3 requires two digits.




A	B	Carry in	Carry out	Sum
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

- The sum output is 1 when only one input is equal to 1, or when all three inputs are equal to 1.
- The carry output is 1 when either two or three of the inputs are equal to 1.

The boolean algebra representation of the two outputs is:

$$\begin{aligned}\text{Sum} &= (A \oplus B) \oplus \text{Carry in} \\ \text{Carry out} &= (A \oplus B) \cdot \text{Carry in} + (A \cdot B)\end{aligned}$$

 To build an adder for **two 8-bit numbers** the **full adder is replicated eight times**.



- The carry out of one full adder is used as the carry in into its left neighbour
- The carry into the rightmost bit is set to 0
- The carry out from the Most Significant Bit sets the OVERFLOW flag in the CPU Status Register

This type of adder is called a **ripple carry adder**  
... because the addition cannot complete until the carry has rippled all the way across the adders.

**SAQ 3.2**

---

1. How many bits does a half adder add?
2. How many bits does a full adder add?
3. Why does a half adder require two outputs?
4. Why does a full adder require two outputs?
5. How would you build an adder to add two 8-bit numbers?

answer

## 4.1 ALU


At the heart of every computer is a processor, or **CPU** (Central Processing Unit)

**CPUs** consist of two main components –

- an **ALU** (Arithmetic and Logic Unit)
- **Control Unit**

We will return to the **control unit** later in the course

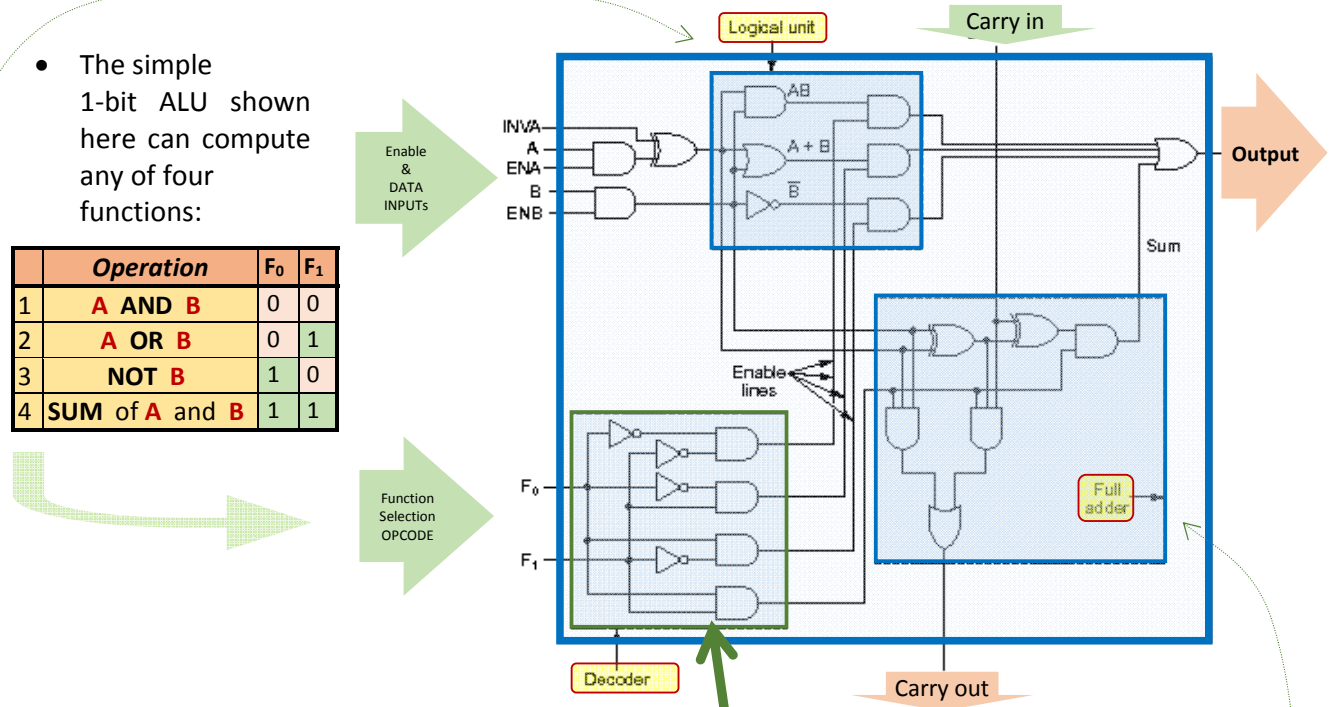The **ALU** is a circuit, used in the **CPU** for performing **Arithmetic and (Boolean) Logical operations**



The **lower left corner** of the **ALU** contains a **2-to-4 Decoder** to generate **enable signals** for the four operations, based on the 2-bit **function control (OPCODE selection) inputs F<sub>0</sub> and F<sub>1</sub>**

- Depending on the values of **F<sub>0</sub>** and **F<sub>1</sub>** one of the outputs of the four functions is passed through to the final **OR** gate for output.

The **upper left corner** of the **ALU** contains the **logic** to compute **A AND B**, **A OR B**, and **NOT B**, but only one of these results is passed onto the final **OR** gate, depending on the enable signal produced by the decoder

- Only one decoder output will be **1**, and so only one of the four **AND** gates that are inputs to the final **OR** gate will output a **1**; the other three will output a **0**.

As well as being able to use **A** and **B** as inputs for logical and arithmetic operations,


- it is possible to force either one to **0** by negating **ENA** or **ENB**.
- It is also possible to produce  $\bar{A}$  by setting **INVA**.
- Under normal circumstances **ENA** and **ENB** are both **1** to enable both inputs and **INVA** is **0**. Under such conditions **A** and **B** are fed into the logic unit unmodified.

The **lower right corner** of the **ALU** contains a full adder for computing the sum of **A** and **B**.

- The full adder also handles the **carries**, because it is possible that several of these circuits will be connected together to perform addition of larger numbers.

Such **1-bit ALUs** allow computer designers to build an **ALU** of any desired size.

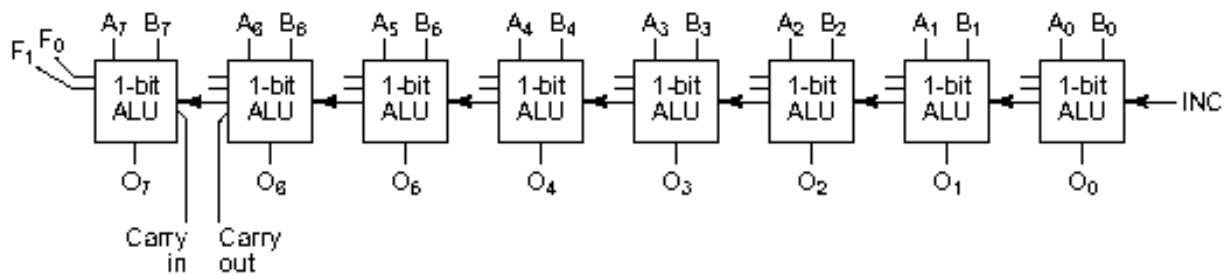- Below is an **8-bit ALU** built of **eight 1-bit ALUs**
  - The **INC** signal is used for addition operations
    - When present it increments (**adds 1**) to the result, allowing the computation of sums such as **A+1**



---

#### SAQ 4.1

- What is the purpose of an ALU?
- What are the three main components of a simple 1-bit ALU?

answer

## 4.2 Memory

Combinational circuits have the property that *their outputs are wholly dependent on their inputs*.

There is another class of circuit that is *sequential* in nature.

- *Sequential circuits* have the property that their *outputs depend not only on present input values, but also on past input values*.

### 4.2.1 Flip-Flops

A *flip-flop* is a sequential circuit that forms the basic building block of memory.


A *flip-flop stores a single bit* by producing an output of a **0** or **1** until changed by conditions on the input(s).

- The term *flip-flop* comes from the operation of the flip-flop – the output *flips* from a **0** to a **1** or *flops* from **1** to a **0**.
- The *output of a flip-flop* is given the identification letter **Q**.

There are several types of flip-flop, but only the *D-type flip-flop* will be discussed here.
 
### 4.2.2 D-type Flip-Flops

Flip-flops are fundamental components of logic systems and so have a standard symbol to denote them. The symbol for a D-type flip-flop is shown below.




A *D-type flip-flop* has two inputs, **D** and **EN**.

- The **D** input is referred to as the *data* input and is the data that the flip-flop is to store.
- The **EN** input is referred to as the *enable* input.
- In a flip-flop the output **Q** only changes on the activating transition of the **EN** signal from one specified logic level to the other logic level.
- Without an *activating transition of the EN signal* the output *will not change even if the input D does*. : In this situation the output remains constant until the next activating transition.
  - This is referred to as *edge triggering*.
  - In *positive edge triggering*, the activating transition is from a **0** to a **1**.
  - In *negative edge triggering*, the activating transition is from a **1** to a **0**.

Both forms are common in flip-flops.

 For simplicities sake we will assume that positive edge triggering is being used.



**D Type flip-flop constructed from logic gates**

The operation of the **D-type flip-flop** can be clarified by a simplified truth table.

EN	D	Q
0	0	Q
0	1	Q
1	0	0
1	1	1

- When **EN** is **0** the input to the two **AND** gates is **0** and so the **S** and **R** inputs to the two **NOR** gates are also set to **0**.
  - This means that the value of **Q** cannot change and remains constant.
- When **EN** is **1** the **S** input is connected to **D** and the **R** input to  $\overline{D}$ .
  - This means that the value on the **D** input is passed through to the output **Q**.
- When **EN** returns to **0** the output **Q** is held constant at the last value of input **D** until the next activating transition of the **EN** signal.


### 4.2.3 Registers

As well as an **ALU**, a **CPU** also contains a **small, high-speed memory used to store temporary results and control information**.

This memory is made up of a number of **registers**, with each register being able to hold one number, up to a maximum size determined by the size of the register.

A flip-flop can store one binary digit. To store eight bits, eight flip-flops must be combined.

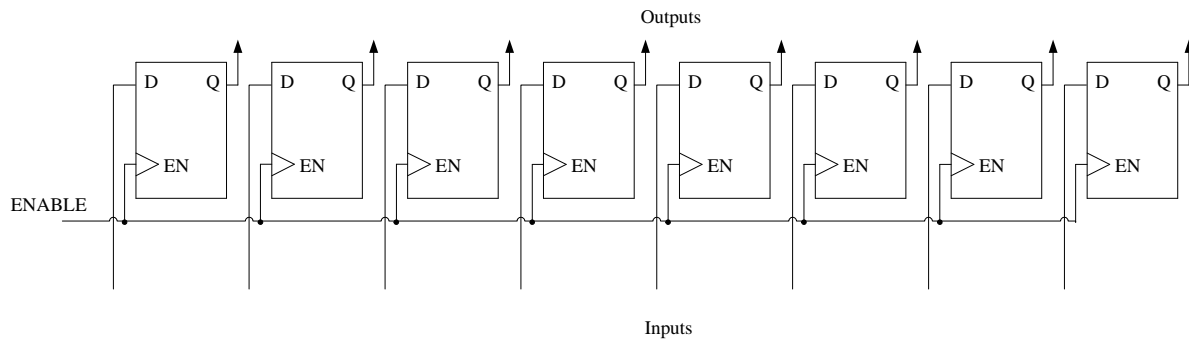The diagram below shows **eight flip-flops combined** into an 8-bit **register**.



- When **EN** is **0** the flip-flops do not record the data being input to them and their **Q** outputs remain unchanged.
- When a device wishes to transfer its data to the flip-flops it sends it's data to the inputs and then creates an activating transition of the **EN** signal ( **EN becomes 1** ).
  - The flip-flops then store the data on their inputs.
- When **EN** returns to **0** the data remains frozen in the flip-flops.
  - Registers will be returned to later in the course.

#### SAQ 4.2

1. What is the difference between a combinational circuit and a sequential circuit?
2. What is the purpose of a flip-flop?
3. When does the output of a flip-flop change?
4. What is a register?

answer

**References**

<http://ece-research.unm.edu/pollard/classes/338/lademo/LookAheadDemo.htm>

---

