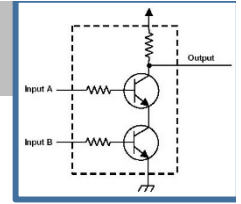


## 2. Combinational Circuits

### Aims

- to show how logic gates are combined on a chip
- to show how logic gates can be combined to produce useful circuits such as :-  
*multiplexors*      and      *comparators*



# 2.0 Introduction



- Gates are made from TRANSISTOR circuits
  - Transistors **AMPLIFY** or **SWITCH** electrical signals. Gates use the **SWITCHING** property
- Gates are not manufactured individually but in units called **integrated circuits** (**ICs** or **chips**)
- Chips can be divided into rough classes based on the *number of gates* they contain :-

<b>SSI</b>	(Small Scale Integrated)	circuit	1 to 10	logic gates
<b>MSI</b>	(Medium Scale Integrated)	circuit	10 to 100	logic gates
<b>LSI</b>	(Large Scale Integrated)	circuit	100 to 100,000	logic gates
<b>VLSI</b>	(Very Large Scale Integrated)	circuit	> 100,000	logic gates

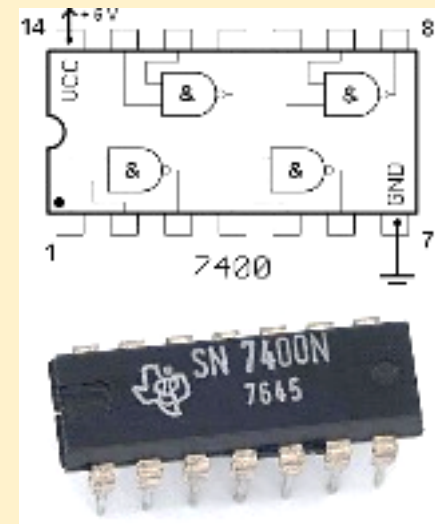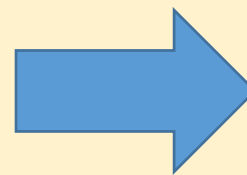In the 1970s, computers were constructed out of large numbers of these chips, but technological advances have allowed an entire CPU to be etched onto a single chip



Fairchild '74' series chip, 1969

*The current state of the art allows nearly  
**10 million gates** on a chip*

## 2.1 Combinational Circuits


Many circuits have the property of their outputs being wholly dependent on their inputs

Such circuits are called ***combinational circuits***

Over the next few weeks we will examine some frequently used combinational circuits

## 2.1.1

# Multiplexors

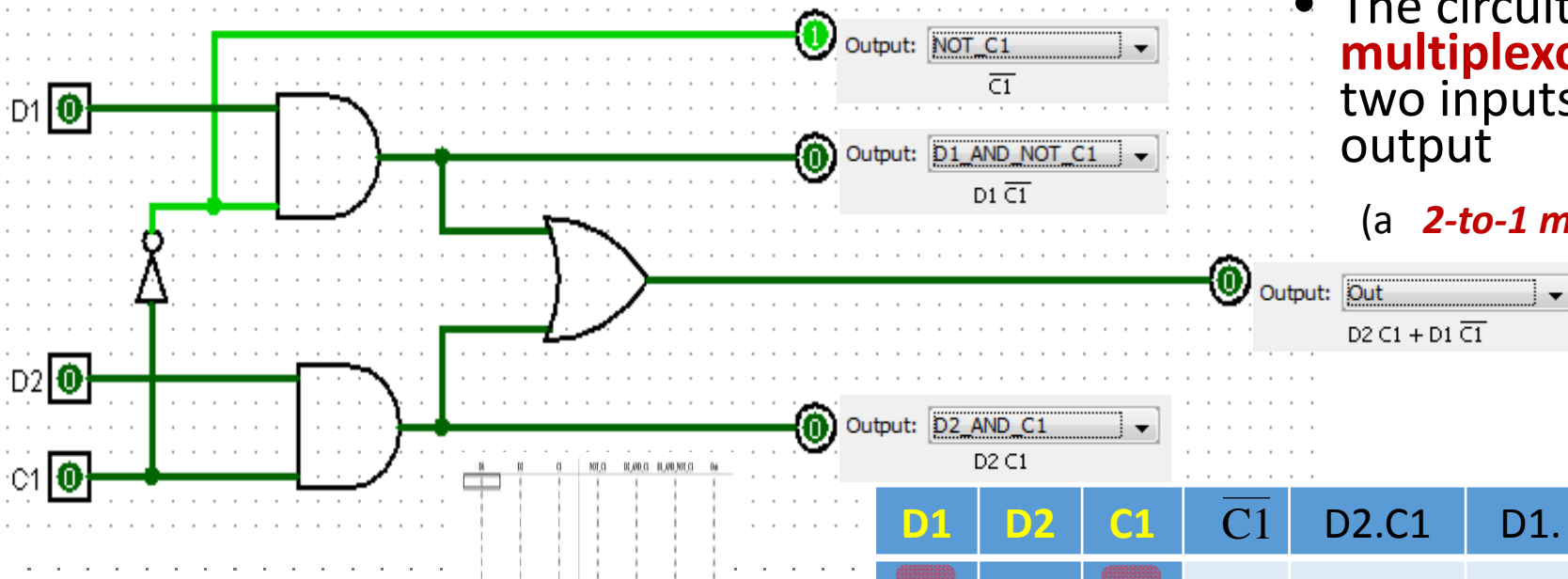

- The circuit (left) is a **multiplexor** with two inputs and one output  
(a **2-to-1 multiplexor**)

D1	D2	C1	Out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

D1	D2	C1	$\overline{C1}$	$D2.C1$	$D1. \overline{C1}$	Out
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	1	0	1	0	0	0
0	1	1	0	1	0	1
1	0	0	1	0	1	1
1	0	1	0	0	0	0
1	1	0	1	0	1	1
1	1	1	0	1	0	1

- If you carefully examine the truth table you can see that the **MULTIPLEXER** output is
- either **D1** or **D2**, depending on the value of **C1**

The **MULTIPLEXER** is acting as a **DATA SWITCH**

D1	D2	C1	Out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

- The truth table reduces to :-

C1	Out
0	D1
1	D2


- The function of a **multiplexor** is to

**route one of many data inputs to a single output**


The control input (**C1**) determines which of the data inputs is passed through to the output

A  $2^n - \text{to} - 1$  multiplexor has  $2^n$  data inputs and  $n$  control inputs.

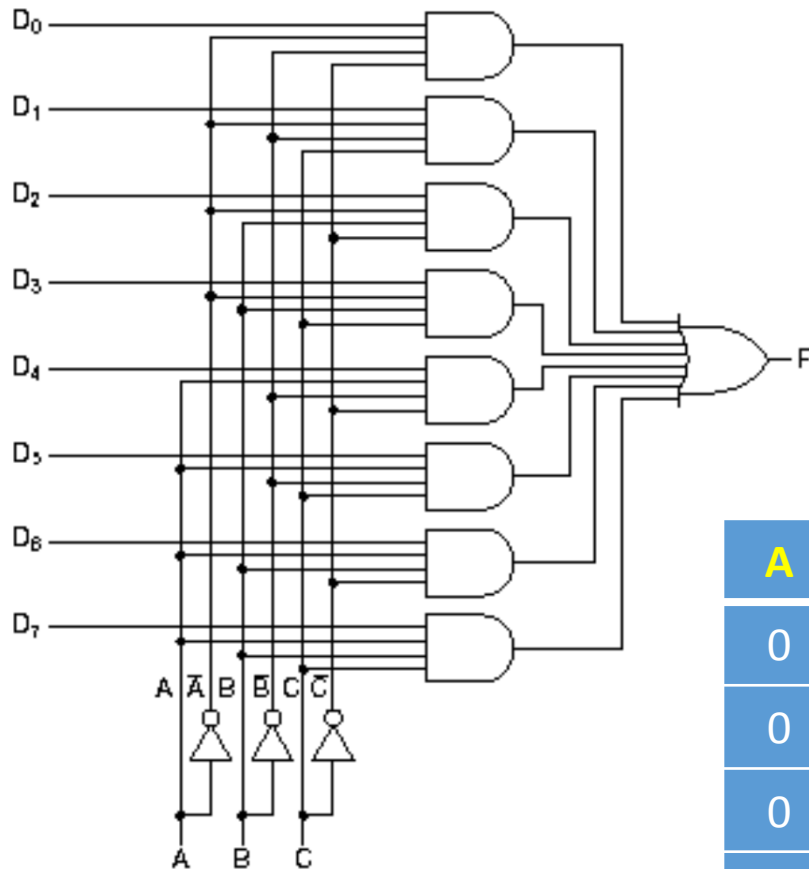
- The bit combination on the control inputs determines which data input is selected for output



A	B	C	Output
0	0	0	$D_0$
0	0	1	$D_1$
0	1	0	$D_2$
0	1	1	$D_3$
1	0	0	$D_4$
1	0	1	$D_5$
1	1	0	$D_6$
1	1	1	$D_7$

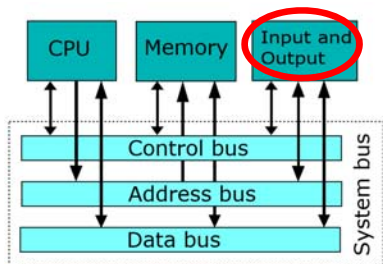

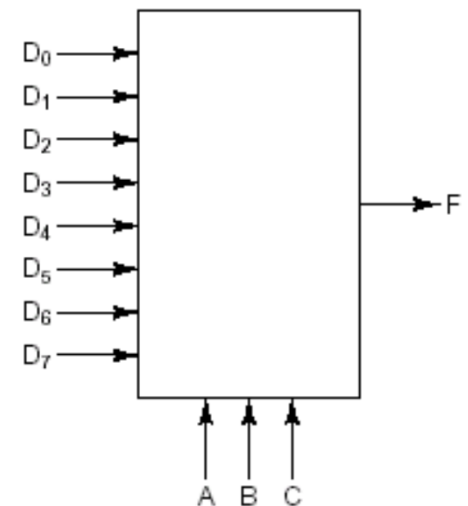
A simpler way to diagrammatically represent an **eight-input multiplexor** is shown below.



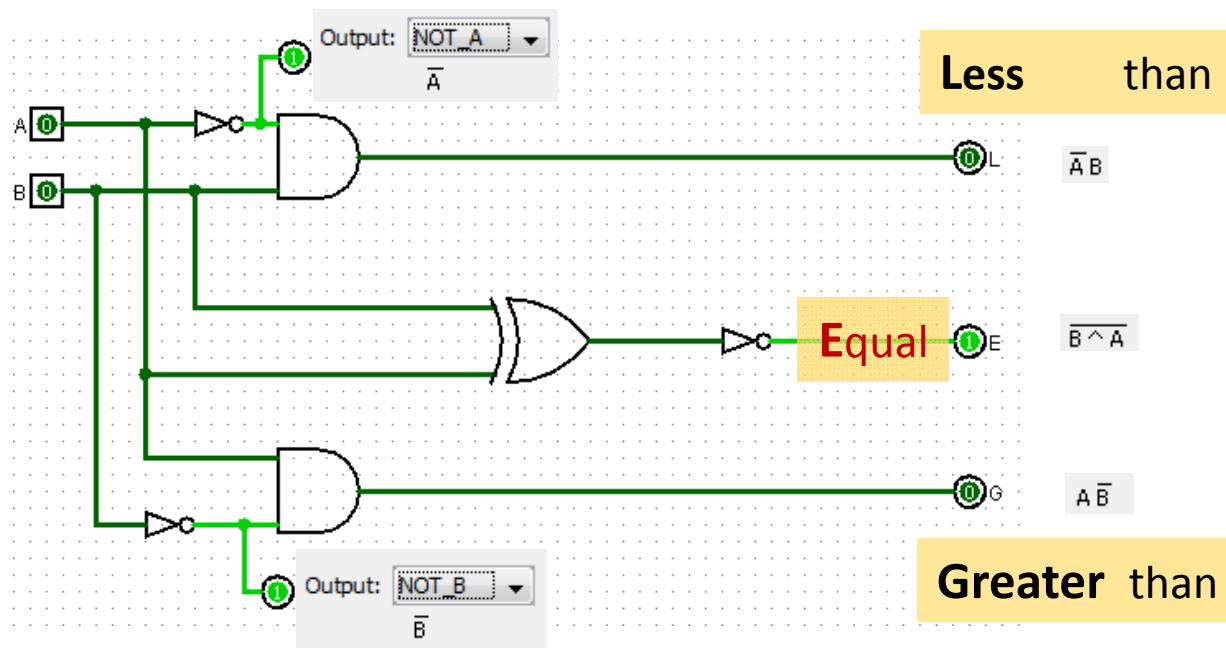
## 2.2 Comparators

- A **comparator** compares **two** inputs


and outputs a **1** on the **E** output if the inputs are **Equal**



A	B	$\bar{A}$	$\bar{B}$	L	E	G
0	0	1	1	0	1	0
0	1	1	0	1	0	0
1	0	0	1	0	0	1
1	1	0	0	0	1	0

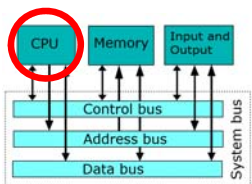

## Multiple (parallel) Bit EQUAL function

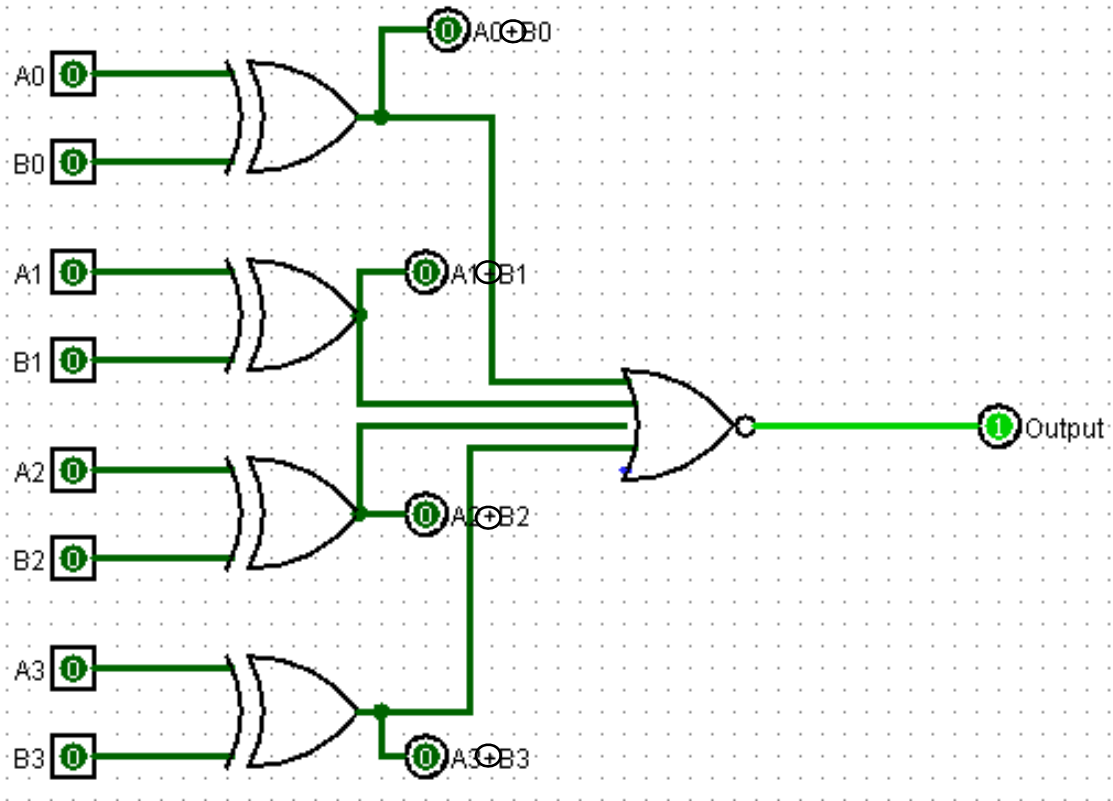[illegible]

A0	B0	A1	B1	A2	B2	A3	B3	$A0 \oplus B0$	$A1 \oplus B1$	$A2 \oplus B2$	$A3 \oplus B3$	NOR
0	0	0	0	0	0	0	0	0	0	0	0	1
0	1	0	1	0	1	0	1	1	1	1	1	0
1	0	1	0	1	0	1	0	1	1	1	1	0
1	1	1	1	1	1	1	1	0	0	0	0	1



# REFERENCES

- <http://worldclassprogramme.com/Arithmetic-Circuits.php>