

6. The Karnaugh Map

Aims

- to describe the *Karnaugh map* technique for circuit simplification
- to apply **Karnaugh** mapping as a technique
- to extend *Karnaugh maps* to include *don't care* states

6.0 Introduction

- Consider the truth table below :-

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

- In **Sum of Products** representation, the truth table can be expressed as :-

$$X = \overline{A}.B.\overline{C} + \overline{A}.B.C + A.\overline{B}.C + A.B.C$$

$$\overline{A}B\overline{C} \wedge \overline{A}BC \wedge A\overline{B}C \wedge ABC$$

		C, D			
		00	01	11	10
A, B	00	0	0	0	0
	01	1	1	1	1
	11	0	0	1	1
	10	0	0	1	1

$\overline{A}B + AC$

A	B	C	D	X
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

Using **Boolean algebra** the expression can be reduced as follows :-

Law name	AND form	OR form
Identity	$1A = A$	$0 + A = A$
Null	$0A = 0$	$1 + A = 1$
Idempotent	$AA = A$	$A + A = A$
Inverse	$A\bar{A} = 0$	$A + \bar{A} = 1$
		$\overline{\bar{A}} = A$
Commutative	$AB = BA$	$A + B = B + A$
Associative	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
Absorption	$A(A + B) = A$	$A + AB = A$ $A + \bar{A}B = A + B$
De-Morgan's	$\overline{AB} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A}\bar{B}$

$$X = \bar{A}\bar{B}\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC$$

$$X = \bar{A}\bar{B}\bar{C} + \bar{A}BC + AC(\bar{B} + B)$$



distributive

OR

$$X = \bar{A}\bar{B}\bar{C} + \bar{A}BC + AC(1)$$



inverse

OR

$$X = \bar{A}\bar{B}\bar{C} + \bar{A}BC + AC$$



identity

AND

$$X = \bar{A}B(\bar{C} + C) + AC$$



distributive

OR

$$X = \bar{A}B(1) + AC$$



inverse

OR

$$X = \bar{A}B + AC$$



identity

AND

- Relatively straightforward for simple circuits.

⇒ But using Boolean algebra to reduce circuits can be difficult.

6.1 Karnaugh Maps

- **Visual way of detecting redundancy in a Sum of Products expression.**
 ⇒ can easily be used for circuits with 2, 3, or 4 inputs.
- **Consists of an array of cells, each representing a possible combination of inputs.**
 ⇒ cells are arranged so that each cell's input combination differs from adjacent cells by only a single bit.

2-input

00	01
10	11

3-input

000	001	011	010
100	101	111	110

4-input

0000	0001	0011	0010
0100	0101	0111	0110
1100	1101	1111	1110
1000	1001	1011	1010

- Now let's look at empty Karnaugh Map tables – ready for logical inputs to be written in them.

2-input

		B	
		0	1
A	0		
	1		

3-input

		BC			
		00	01	11	10
A	0				
	1				


4-input

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				

NOTICE !!

- Karnaugh Map Numbers do not follow a binary sequence

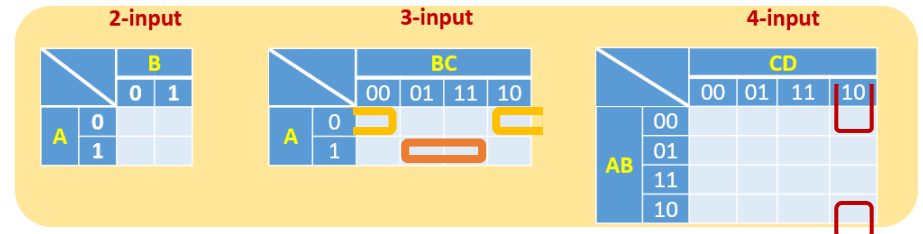⇒ Rows and columns are arranged so that **only a single bit changes between neighbours**
 ⇒ this applies at the edges too




Building a Karnaugh Map from a Truth Table

Starting with an empty *Karnaugh map* ...

- locate the **1's** in the function's **truth table** output




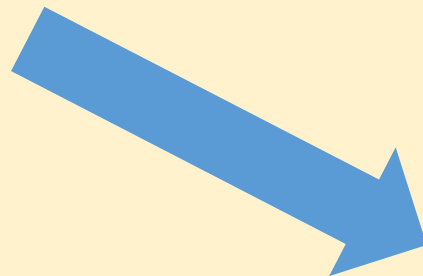- place them in the cells corresponding to the same inputs



A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

		BC			
		00	01	11	10
A	0	0	0	1	1
	1	0	1	1	0

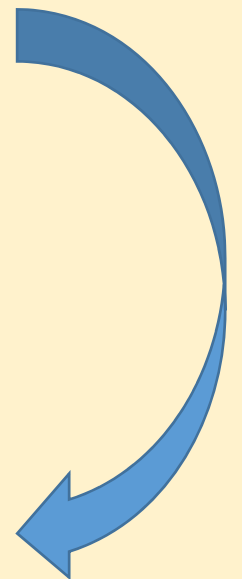

Karnaugh Map RULES

1. Group adjacent 1's together in **square** or **rectangular groups** of **2, 4, 8, or 16**, such that the total number of groups and isolated 1's is minimised, ... while making the largest groups as possible

1. Groups may overlap so that a particular cell may be included in more than one group

3. Remember that **adjacency wraps around the edges of the map**

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

- Considering the grouping, notice the following :

1. **B** changes but the output does not
 - Therefore **B** is redundant in this group
2. **C** changes but the output does not
 - Therefore **C** is redundant in this group

		B, C			
		00	01	11	10
A	0	0	0	0	1
	1	0	1	0	0

$\bar{A}B\bar{C} + A\bar{B}C$

- Boolean expressions are written for each group, leaving out the redundant terms

$$X = \bar{A}.B + A.C$$


- Process of converting a truth table output into a **Karnaugh map** can be summarised into a basic set of rules :

1. Each cell with a **1** must be included in at least one group
2. Form the **largest possible groups**
3. Form as **few groups as possible**
4. Groups may be sizes that are powers of **2**
5. Groups may be **square** or **rectangular** only
(including **wrap-around** at the map edges)
6. The **larger a group is, the more redundant inputs there are** : -
 - A group of **1** has **no** redundant inputs
 - A group of **2** has **1** redundant input
 - A group of **4** has **2** redundant inputs
 - A group of **8** has **3** redundant inputs
 - A group of **16** has **4** redundant inputs

2-Input

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

	B	
	0	1
A	0	1
1	1	

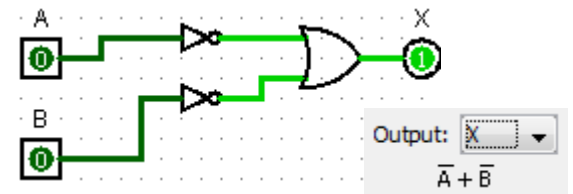

$$X = \bar{B} + \bar{A}$$

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

Output:
 Format:


		B	
		0	1
A	0	1	1
	1	1	0

$\bar{A} + \bar{B}$

3-Input

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

		BC			
		00	01	11	10
A	0			1	1
	1	1		1	1

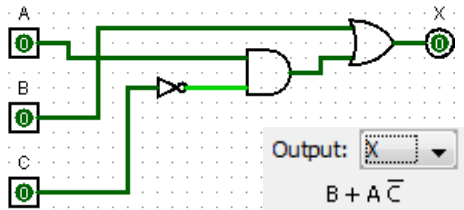

$$X = A.\bar{C} + B$$

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Output:
 Format:

B, C


		00	01	11	10
A	0	0	0	1	1
	1	1	0	1	1

B + A \bar{C}



4-Input

A	B	C	D	X
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

A	B	C	D	X
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

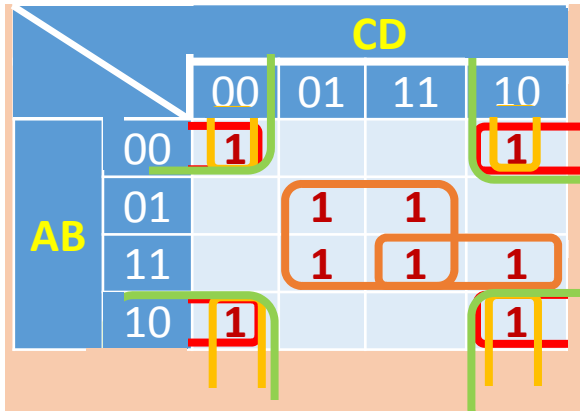
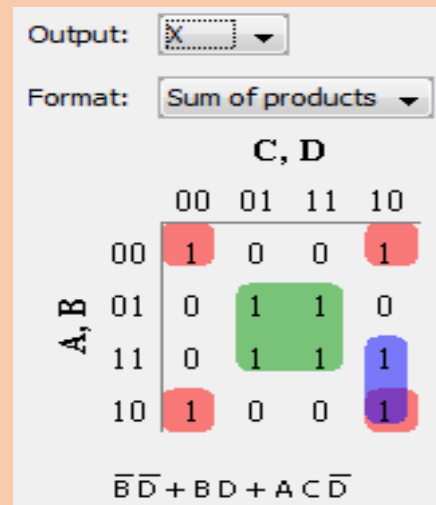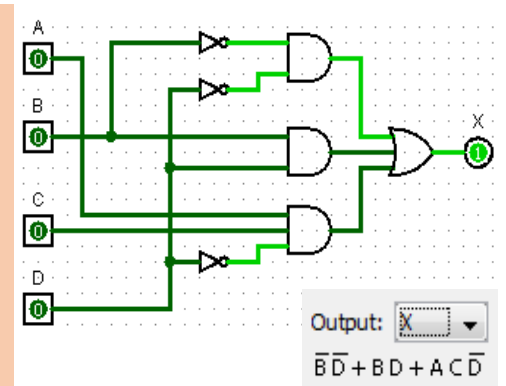
$$X = \overline{B}.\overline{D} + B.D + A.C.\overline{D}$$



A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Output:


Format:

B, C

		00	01	11	10
A	0	1	1	1	1
	1	0	0	1	0

$\bar{A} + BC$

$$X = \bar{A} + B.C$$

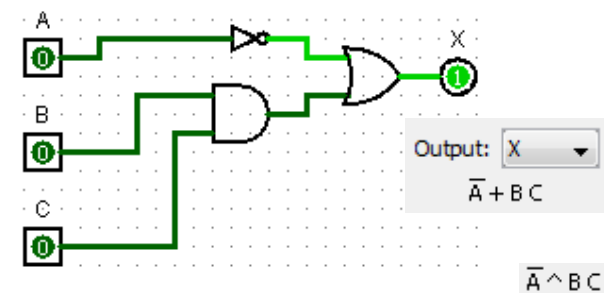

A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Output:


Format:

B, C

		00	01	11	10
A	0	0	1	1	0
	1	0	1	1	0

C

$$X = C$$

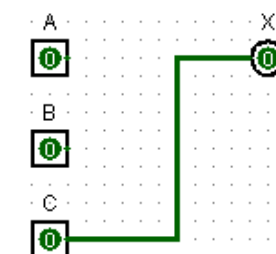

A	B	C	D	X
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

Output:


Format:

C, D

		00	01	11	10
A, B	00	1	1	1	1
	01	1	0	0	1
	11	1	0	0	1
	10	1	0	0	1

$\bar{A}\bar{B} + \bar{D}$

$$X = \bar{D} + \bar{A}.\bar{B}$$

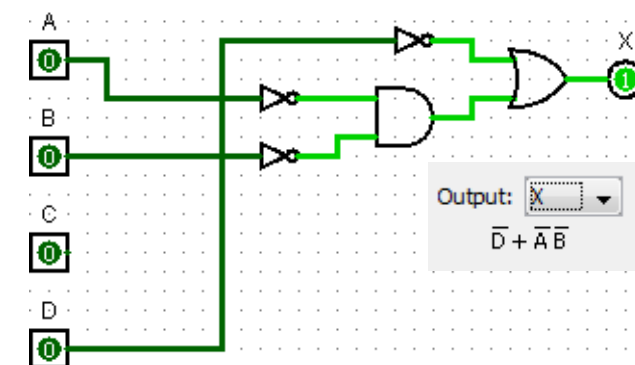

7.1 Don't Care Logic States

We have seen how :-


Karnaugh maps are a visual way of detecting redundancy in a Sum of Products representation

⇒ We sometimes have cases where the output of a circuit does not matter

⇒ Certain input combinations for which we **do not care** what the output is

Don't Care States

- Consider a seven-segment display:

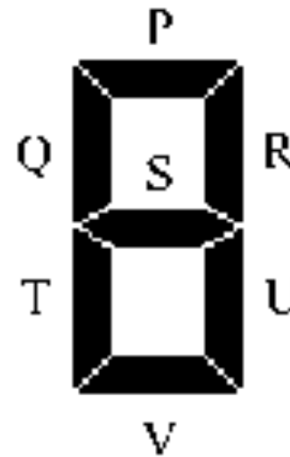

- Only the numbers 0 to 9 can be displayed.

⇒ **four bits** are required :-

0000

represents **zero**

1001

represents **nine**

9

- **Four bits** can actually represents values from **0** (0000) to **15** (1111).

⇒ when the input bit values are from **10** (1010) to **15** (1111)

we do not care what the output is



⇒ inputs to the circuits will never have those values so
what the circuit does if it does happen

we do not care

- Consider the segment labelled **P**.

⇒ assume that a value of **1** *activates the segment* and a value of **0** *turns it off*

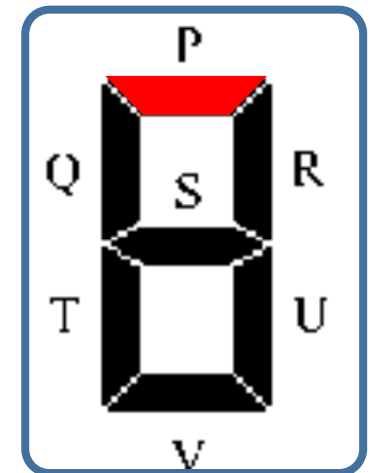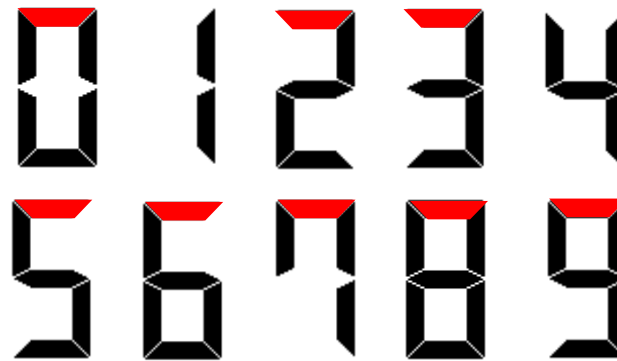⇒ the top segment will be lit for values **0, 2, 3, 5, 6, 7, 8, 9**



⇒ We *do not care* what it does if the inputs are in the range **10** to **15**

- In both the truth table and the Karnaugh map, a don't care state is represented with a '**d**'.
They are drawn on the Karnaugh map along with the **1**'s

'X' is also a common 'don't care' notation

For segment 'P'



A	B	C	D	P
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	d
1	0	1	1	d
1	1	0	0	d
1	1	0	1	d
1	1	1	0	d
1	1	1	1	d


		CD			
		00	01	11	10
AB	00	1		1	1
	01		1	1	1
	11	d	d	d	d
	10	1	1	d	d

A	B	C	D	P
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	x
1	0	1	1	x
1	1	0	0	x
1	1	0	1	x
1	1	1	0	x
1	1	1	1	x

		C, D			
		00	01	11	10
A, B	00	1	0	1	1
	01	0	1	1	1
	11	x	x	x	x
	10	1	1	x	x

$\overline{B}\overline{D} + C + BD + A$
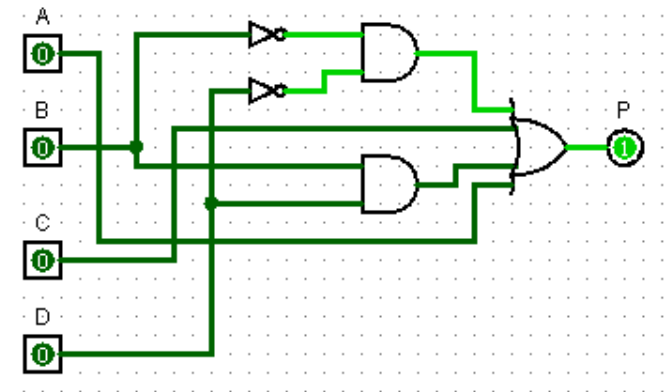
$$P = A + C + B.D + \overline{B}.\overline{D}$$



Example

A	B	C	D	X	Y	Z
0	0	0	0	1	1	1
0	0	0	1	1	0	0
0	0	1	0	0	0	1
0	0	1	1	1	1	0
0	1	0	0	0	1	1
0	1	0	1	1	1	0
0	1	1	0	0	0	1
0	1	1	1	1	1	0
1	0	0	0	0	1	1
1	0	0	1	1	0	1
1	0	1	0	1	0	1
1	0	1	1	1	1	1
1	1	0	0	d	d	d
1	1	0	1	d	d	d
1	1	1	0	d	d	d
1	1	1	1	d	d	d

A	B	C	D	X	Y	Z
0	0	0	0	1	1	1
0	0	0	1	1	0	0
0	0	1	0	0	0	1
0	0	1	1	1	1	0
0	1	0	0	0	1	1
0	1	0	1	1	1	0
0	1	1	1	1	1	0
1	0	0	0	0	1	1
1	0	0	1	1	0	1
1	0	1	0	1	0	1
1	0	1	1	1	1	1
1	1	0	0	x	x	x
1	1	0	1	x	x	x
1	1	1	0	x	x	x
1	1	1	1	x	x	x

X

		CD			
		00	01	11	10
AB	00	1	1	1	
	01		1	1	
	11	d	d	d	d
	10		1	1	1

Output:

Format:

C, D

		00	01	11	10
A, B	00	1	1	1	0
	01	0	1	1	0
	11	x	x	x	x
	10	0	1	1	1

$\overline{A}\overline{B}\overline{C} + D + AC$

$$X = \overline{A}\overline{B}\overline{C} + D + AC$$

Output:

$\overline{A}\overline{B}\overline{C} + D + AC$

Example

A	B	C	D	X	Y	Z
0	0	0	0	1	1	1
0	0	0	1	1	0	0
0	0	1	0	0	0	1
0	0	1	1	1	1	0
0	1	0	0	0	1	1
0	1	0	1	1	1	0
0	1	1	0	0	0	1
0	1	1	1	1	1	0
1	0	0	0	0	1	1
1	0	0	1	1	0	1
1	0	1	0	1	0	1
1	0	1	1	1	1	1
1	1	0	0	d	d	d
1	1	0	1	d	d	d
1	1	1	0	d	d	d
1	1	1	1	d	d	d

A	B	C	D	X	Y	Z
0	0	0	0	1	1	1
0	0	0	1	1	0	0
0	0	1	0	0	0	1
0	0	1	1	1	1	0
0	1	0	0	0	1	1
0	1	0	1	1	1	0
0	1	1	1	1	1	0
1	0	0	0	0	1	1
1	0	0	1	1	0	1
1	0	1	0	1	0	1
1	0	1	1	1	1	1
1	1	0	0	x	x	x
1	1	0	1	x	x	x
1	1	1	0	x	x	x
1	1	1	1	x	x	x

Y

		CD			
		00	01	11	10
AB	00	1		1	
	01	1	1	1	
	11	d	d	d	d
	10	1		1	

Output:

Format:

		C, D			
		00	01	11	10
A, B	00	1	0	1	0
	01	1	1	1	0
	11	x	x	x	x
	10	1	0	1	0

$\overline{C}\overline{D} + CD + B\overline{C}$

$$Y = \overline{C}.\overline{D} + C.D + B.D$$

Output:

$\overline{C}\overline{D} + CD + B\overline{C}$

Example

A	B	C	D	X	Y	Z
0	0	0	0	1	1	1
0	0	0	1	1	0	0
0	0	1	0	0	0	1
0	0	1	1	1	1	0
0	1	0	0	0	1	1
0	1	0	1	1	1	0
0	1	1	0	0	0	1
0	1	1	1	1	1	0
1	0	0	0	0	1	1
1	0	0	1	1	0	1
1	0	1	0	1	0	1
1	0	1	1	1	1	1
1	1	0	0	d	d	d
1	1	0	1	d	d	d
1	1	1	0	d	d	d
1	1	1	1	d	d	d

A	B	C	D	X	Y	Z
0	0	0	0	1	1	1
0	0	0	1	1	0	0
0	0	1	0	0	0	1
0	0	1	1	1	1	0
0	1	0	0	0	1	1
0	1	0	1	1	1	0
0	1	1	0	0	1	1
0	1	1	1	1	1	0
1	0	0	0	0	1	1
1	0	0	1	1	0	1
1	0	1	0	1	0	1
1	0	1	1	1	1	1
1	1	0	0	x	x	x
1	1	0	1	x	x	x
1	1	1	0	x	x	x
1	1	1	1	x	x	x

Z

		CD			
		00	01	11	10
AB	00	1			1
	01	1			1
	11	d	d	d	d
	10	1	1	1	1

Output:

Format:

C, D

		00	01	11	10
A, B	00	1	0	0	1
	01	1	0	0	1
	11	x	x	x	x
	10	1	1	1	1

$\bar{D} + A$

$$Z = \bar{D} + A$$

Output:

$\bar{D} + A$

The circuit for X, Y, Z

A	B	C	D	X	Y	Z
0	0	0	0	1	1	1
0	0	0	1	1	0	0
0	0	1	0	0	0	1
0	0	1	1	1	1	0
0	1	0	0	0	1	1
0	1	0	1	1	1	0
0	1	1	0	0	1	1
0	1	1	1	1	1	0
1	0	0	0	0	1	1
1	0	0	1	1	0	1
1	0	1	0	1	0	1
1	0	1	1	1	1	1
1	1	0	0	x	x	x
1	1	0	1	x	x	x
1	1	1	0	x	x	x
1	1	1	1	x	x	x

$$X = \overline{A}.\overline{B}.\overline{C} + D + A.C$$

$$Y = \overline{C}.\overline{D} + C.D + B.D$$

$$Z = \overline{D} + A$$

